



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Mock Midterm Examination

Course: CSE251 Electronic Circuits, Section-X
Instructor: Rashedul Amin Tuhin, Senior Lecturer, CSE Department
Full Marks: 60 (30 will be counted for final grading)
Duration: 80 minutes

Notes: There are **SIX** questions, answer ALL of them. Course Outcome (CO), Cognitive Level, Mark, for each question are mentioned at the right margin.

In the actual exam, the formulas will not be given.

Q1. From the given i-v characteristics graph, **calculate** the following terms: [CO1, C2, Mark: 20]

a) the internal resistance of the diode (r_D) if the series resistance is given as $3k\Omega$. [mark:04]

b) the thermal voltage (V_T) at 27°C . [mark:04]

$$V_T = \frac{K_B T}{q}$$

c) the Scaling Current (I_S). [mark:04]

d) the diode parameter (n). [mark:04]

$$I_D = I_S e^{\left(\frac{V_D}{nV_T}\right)}$$

e) Explain the PWL model equivalent circuit of a diode. [mark: 04]

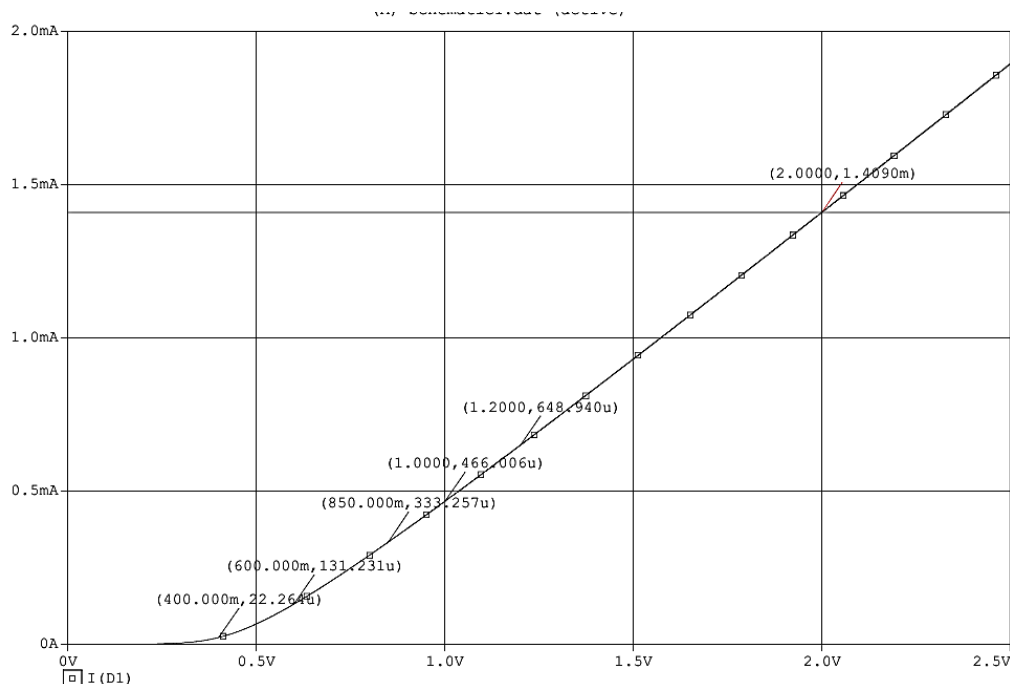


Figure 1

Q2. Assuming the diodes to be ideal, find the values of I and V in the circuits given in Figure 2.

[CO1, C3,
Mark: 12]



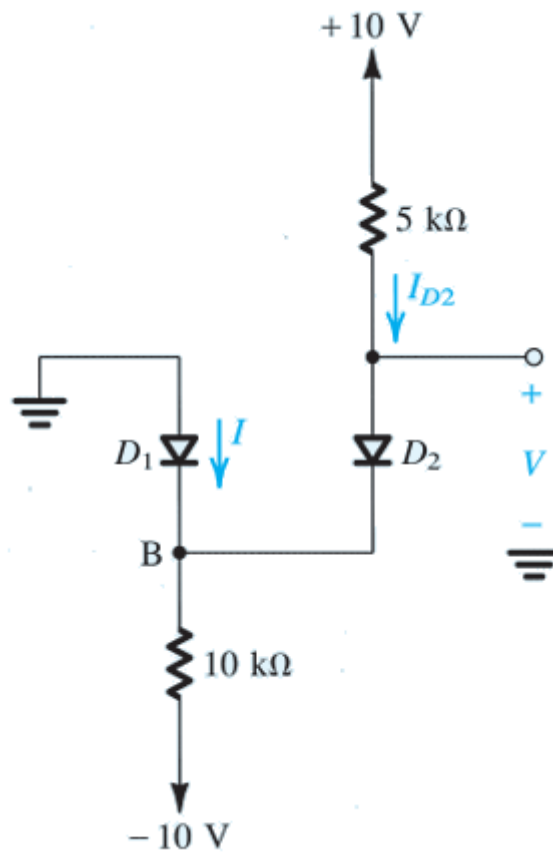


Figure 2

Q3.

[CO2, C3,
Mark: 12]

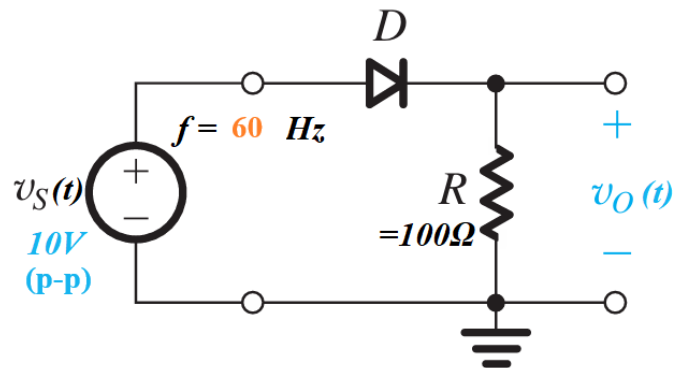

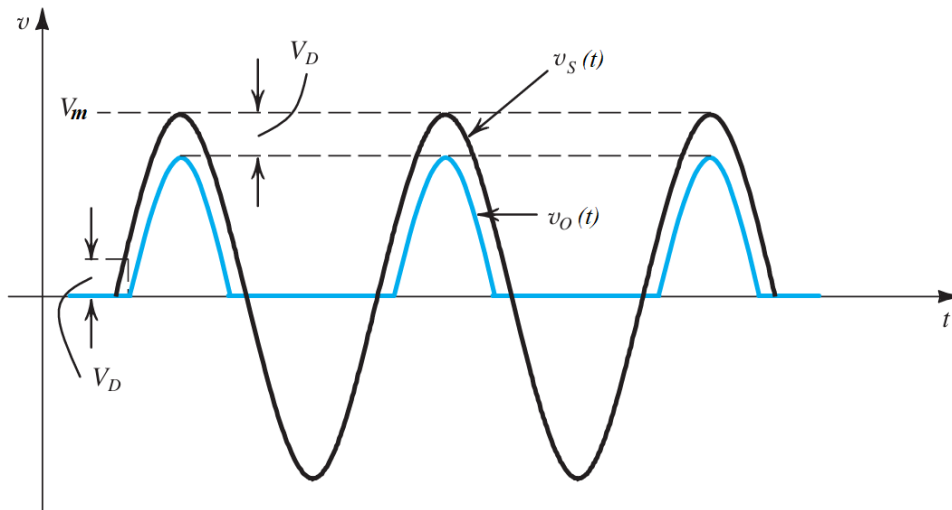

Given,

$$v_s(t) = V_m \sin \omega t = V_m \sin 2\pi f t$$

$$v_s(\Delta t) = V_m \sin \omega \Delta t = V_D = v_s(\theta) = V_m \sin \theta$$

$$\sin \omega \Delta t = \frac{V_D}{V_m} = \sin \theta$$

Consider a simple half wave rectifier with a silicon diode,

- sketch** the output waveforms in the time domain (t) and **mark** the diode conduction time. [mark:02]
- sketch** the output waveforms in the frequency domain (θ) and **mark** the diode conduction angle. [mark:02]
- Show that the average** value of the output voltage in a silicon diode half wave rectifier is $(\frac{V_m}{\pi} - \frac{V_D}{2})$, where the symbols carry their usual meaning.

Calculate the following terms for the half wave rectifier:

- Diode conduction time*, $(\frac{T}{2} - 2\Delta t)$ [mark:02]
- Diode conduction angle*, $(\pi - 2\theta)$ [mark:02]
- Relate among *Diode conduction time* and *Diode conduction angle*. [mark:02]
- Diode conduction percentage*. [mark:02]
- Show** how to use *Diode conduction percentage* to calculate *Diode conduction angle* from *Diode conduction time* and vice-versa.
- Peak Inverse Voltage*, (V_m) [mark:02]
- Peak diode current*, $(\frac{V_m - V_D}{R})$ [mark:02]
- DC Average value* of the output voltage, $(\frac{V_m}{\pi} - \frac{V_D}{2})$ [mark:02]

Q2
*


Repeat the same problem given in Q2 for a silicon diode full wave bridge rectifier.
Draw the circuit diagram.

- sketch** the input and output waveforms in the time domain (t) and **mark** the diode conduction time. [mark:02]

- b) **sketch** the input and output waveforms in the frequency domain (θ) and **mark** the diode conduction angle. [mark:02]
- c) *Diode conduction time*, $(\frac{T}{2} - 2\Delta t)$ [mark:02]
- d) *Diode conduction angle*, $(\pi - 2\theta)$ [mark:02]
- e) *Diode conduction percentage* [mark:02]
- f) *Full cycle diode conduction time*, $(T - 4\Delta t)$ [mark:02]
- g) *Full cycle Diode conduction angle*, $(2\pi - 4\theta)$ [mark:02]
- h) *Full cycle conduction percentage* $(\frac{T-4\Delta t}{T} \times 100\%)$ [mark:02]
- i) *Peak Inverse Voltage*, $(V_m - V_D)$ [mark:02]
- j) *Peak diode current*, $(\frac{V_m - 2V_D}{R})$ [mark:02]
- k) *DC Average value of the output voltage*, $(\frac{2V_m}{\pi} - 2V_D)$ [mark:02]

Q3.

[CO2, C3,
Mark: 06]

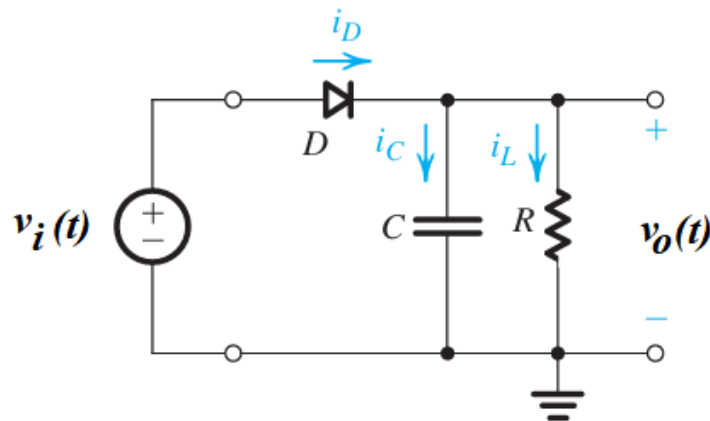

Given that, a peak rectifier circuit with the following parameters,

$$V_D = 0.7V, V_i = 70.7V \text{ (RMS)}, V_r = 5V, R = 100\Omega, f = 60\text{Hz}.$$

Derive the formula to relate between the Ripple voltage (V_r) and the Peak output voltage (V_m).

$$V_r = \frac{V_m}{fCR}$$


Show that the diode conduction angle, $\theta = \omega\Delta t = \sqrt{\frac{2V_r}{V_m}}$ when $V_r \ll V_m$.

Calculate the following terms:

- a) the value of the capacitor for the peak rectifier. [mark:02]
- b) the diode conduction angle. [mark:02]
- c) the peak value of the load current. [mark:02]
- d) the average value of the load current. [mark:02]

Q4. The input signal, $v_i(t)$ to the circuit is defined as shown in Figure 1.

[CO2, C3,
Mark: 06]

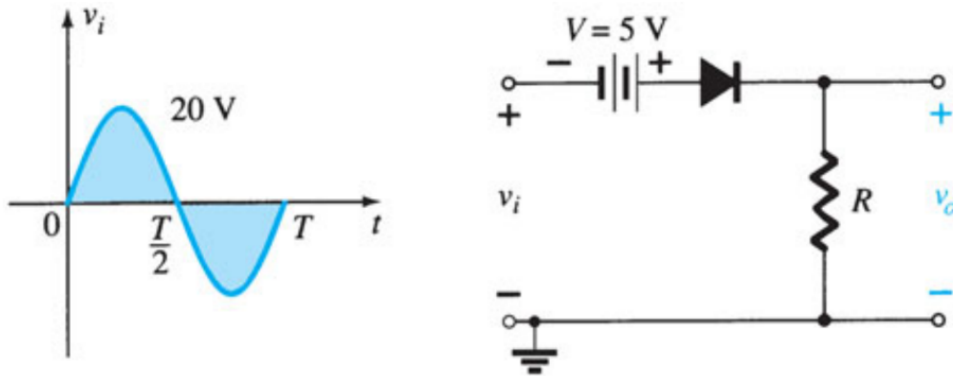

Determine the transition voltage for the clipper circuit.

Sketch the output waveform, $v_o(t)$. Assume the diode to be an ideal diode.

Q5. The input signal, $v_i(t)$ and the circuit are shown in Figure 2.

[CO2, C3,
Mark: 06]

