



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Mock Final Examination

Course: CSE251 Electronic Circuits, Section-X
Instructor: Rashedul Amin Tuhin, Senior Lecturer, CSE Department
Full Marks: 30 (30 will be counted for final grading)
Duration: 90 minutes

Notes: There are **SIX** questions, answer ALL of them. Course Outcome (CO), Cognitive Level, Mark, for each question are mentioned at the right margin.

- Q1.** A 741-op amp has an open-loop voltage gain of 3×10^5 , input resistance of $3 M\Omega$, and output resistance of 60Ω . The op amp is used in the circuit of *Figure 1*. **Find** the closed loop gain $\frac{v_o}{v_i}$. [CO3, C3, Mark: 04]

Using the op-amp equivalent circuit model, **determine** current i when $v_s = 3 V$.

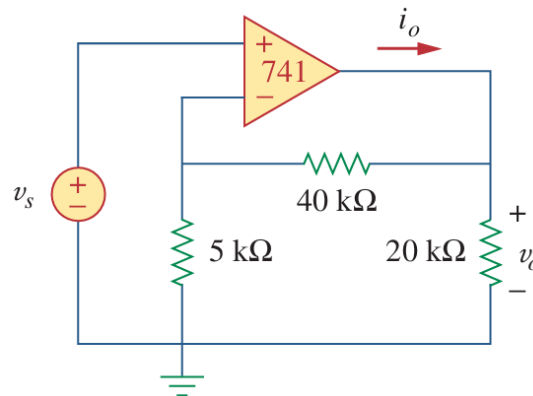


Figure 1

- Q2.** **Design** a circuit using a series of op-amps to generate the following output, [CO3, C4, Mark: 09]
- $$v_o(t) = - \int_0^t (2v_1 - 3v_2 - 3v_3) dt$$

If the integrating capacitor is $C = 1\mu F$, **obtain** other component values.

- Q3.** For an *n-channel enhancement type* MOSFET, [CO1, C2, Mark: 04]
- Draw** the structure and mark the components.
 - Describe** the MOSFET operation when,
 - $V_{GS} = 0 V, V_{DS} = 0 V$
 - $V_{GS} > V_T, V_{DS} = 0 V$
 - $V_{GS} > V_T, V_{DS} > 0 V$
 - Explain** with diagrams how the MOSFET can act as an amplifier.

- Q4.** A $0.18\text{-}\mu\text{m}$ fabrication process is specified to have an *oxide thickness* of 4nm , *electron mobility* of $450\text{cm}^2/\text{V}\cdot\text{s}$, and *threshold voltage* of 0.5V . **Find** the value of the *process transconductance parameter* k_n . [CO1, C3, Mark: 03]

For a MOSFET with *minimum length* fabricated in this process, **find** the required *width* so that the device exhibits a *channel resistance* of 1000Ω when $V_{GS} = 2\text{V}$.

- Q5.** For a $0.18\text{-}\mu\text{m}$ fabrication process for which the *oxide thickness* is given as 4nm , *electron mobility* of $450\text{cm}^2/\text{V}\cdot\text{s}$, **find** the *oxide capacitance per unit area* and the *process transconductance parameter* k_n . [CO2, C3, Mark: 03]

Find the *overdrive voltage* required to operate the MOSFET in the saturation region, where the *aspect ratio* is 20 and *saturation current* is 0.3mA .

- Q6.** For the circuit given in Figure 2, **determine** k_n , I_{DQ} , V_{GSQ} and V_{DS} . [CO2, C4, Mark: 07]

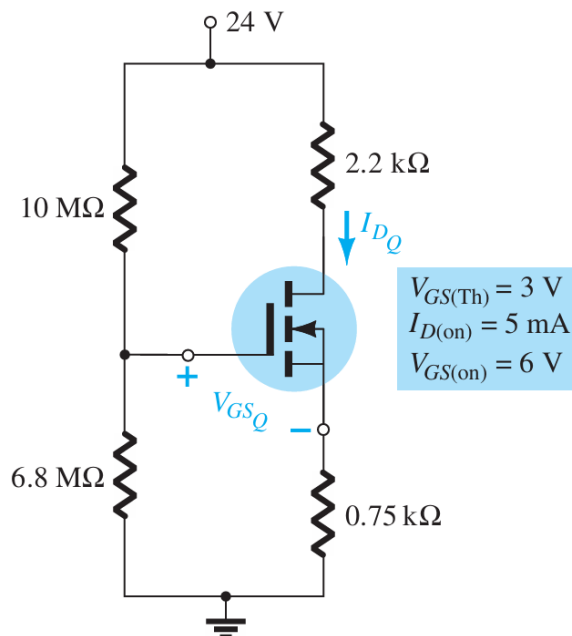


Figure 2