



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Electronic Circuits (CSE251)
Mini Project

Project 1

A. Design and Analysis of a Diode-Based Rectifier Circuit.

Key Tasks

- I. Rectifier Circuits
 - a. Build a full-wave rectifier using a diode bridge (four diodes).
 - b. Add smoothing capacitors and measure ripple voltage at the output.
- II. Measurement and Analysis
 - a. Use an AC signal generator and oscilloscope to observe input and output waveforms.
 - b. Measure peak voltage, ripple voltage, and DC output voltage.
 - c. Calculate rectification efficiency and analyze how diode forward voltage affects output.
- III. Report
 - a. Document circuit diagrams, measurements, waveform screenshots, and analysis.
 - b. Discuss applications of diode rectification in real time.

Project 2

B. Design and Implementation of a BJT-Based AND Logic Gate

Key Tasks

- I. Design the circuit
 - a. Calculate base resistors for each transistor to ensure proper switching.
 - b. Choose a collector load resistor for correct output voltage levels.
- II. Simulate the circuit
 - a. Verify correct AND truth table behavior with logic input combinations (00, 01, 10, 11).
- III. Build the circuit
 - a. Use common NPN transistors (e.g., 2N3904).
 - b. Use a 5 V supply for logic HIGH levels.
- IV. Test and measure
 - a. Apply logic input combinations with switches or a signal generator.
 - b. Measure output voltage levels and confirm logic operation.
 - c. Analyze switching speed and power consumption.
- IV. Report
 - a. Document circuit diagrams, measurements, and analysis.
 - b. Discuss applications of BJT-Based AND Logic Gate in real time.

Project 3

C. Design and Implementation of an Op-Amp Based Precision DC Voltage Amplifier.

Key Tasks

- I. Circuit design
 - a. Calculate resistor values for the desired gain (e.g., gain = 10 or 100).
 - b. Design an offset null circuit using offset null pins if available, or by adding balancing resistors/potentiometers.
- II. Simulation
 - a. Verify gain and offset in SPICE simulation.
- III. Construction
 - a. Build on a breadboard with precision resistors (1% or better).
- IV. Testing
 - a. Use a low-noise DC voltage source and a high-precision multimeter to measure output voltage for known inputs.
- V. Analysis
 - a. Compare measured gain and offset to theoretical values.
 - b. Plot output voltage vs temperature and discuss drift sources and compensation effectiveness.
- VI. Report
 - a. Document circuit diagrams, measurements, waveform screenshots, and analysis.
 - b. Discuss applications of the Op-Amp Based Precision DC Voltage Amplifier in real time.

Grading rubric

- Design correctness and calculations: 40 pts
- Experimental procedure & data quality: 20 pts
- Discussion, error analysis & mitigation: 20 pts
- Documentation: 15 pts
- Report: 5 pts

Project covers the following:

Course Outcome: CO4

Program Outcome: PO1

Cognitive Level: C3

Psychomotor Level: P2, P3

Affective Level: A2

Knowledge Profile: K1, K3

Complex Engineering Problem: EP1, EP2