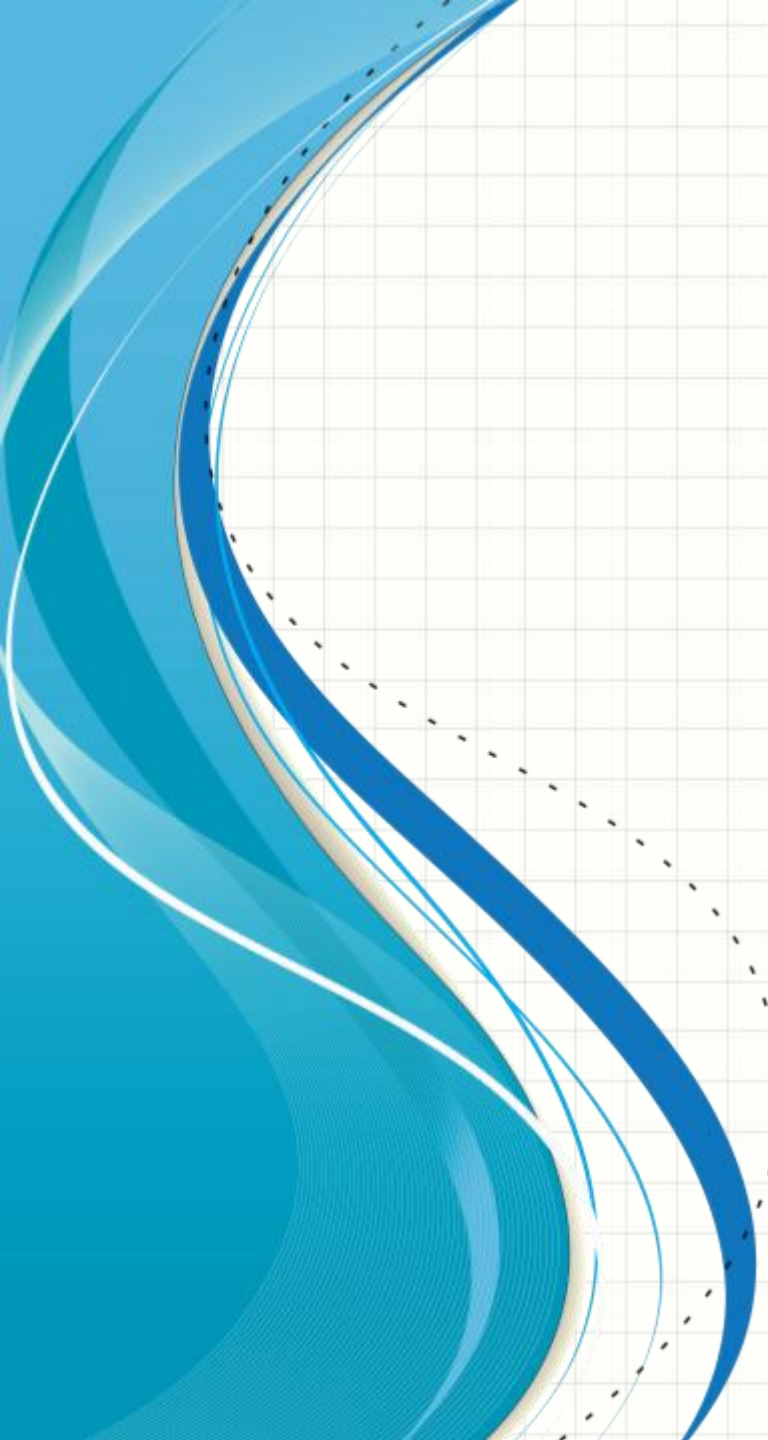




CSE-251

ELECTRONIC CIRCUITS


LECTURE-12

Syed Jamiul Alam
Lecturer
Department of CSE

Today's Overview:


□ *Current Voltage
Characteristics*

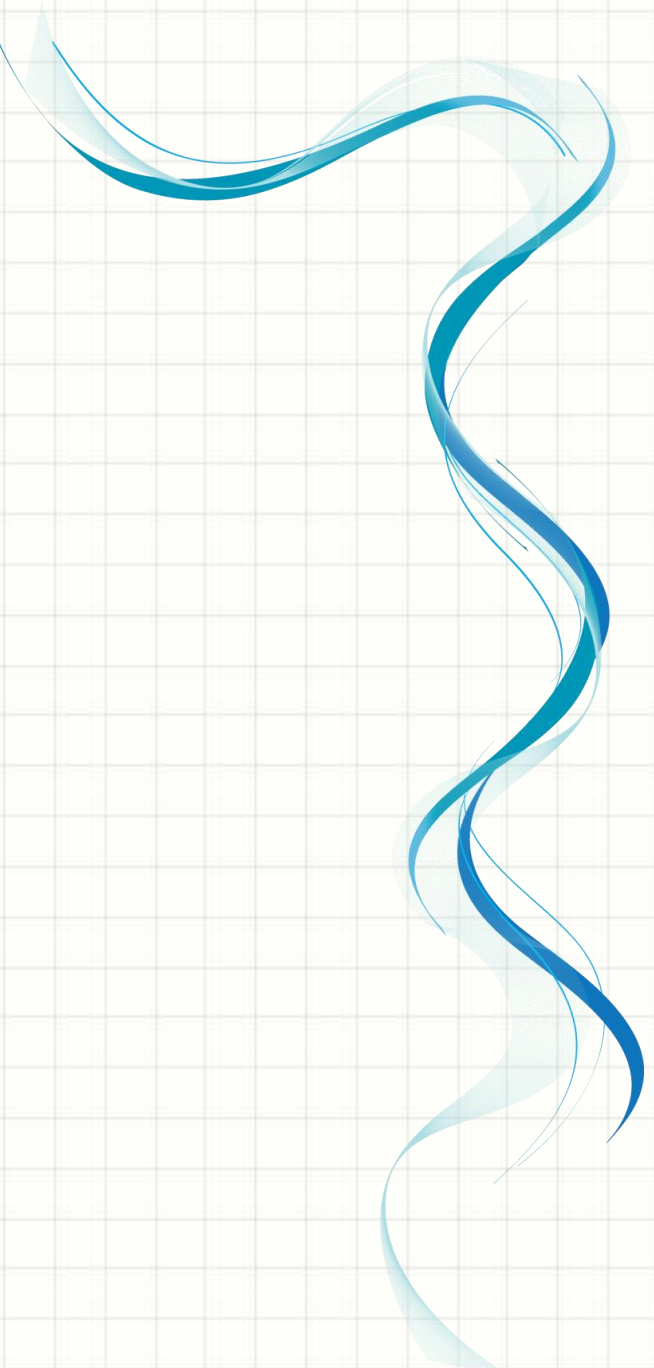

A decorative blue wavy line with a light blue shadow, flowing vertically on the left side of the slide.

Current Voltage Characteristics

Common Base Configuration (n-p-n):

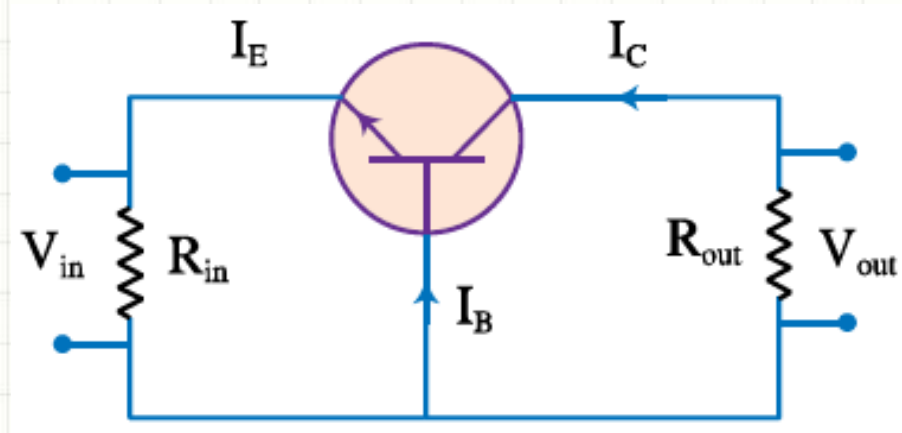

Common Base Configuration (n-p-n):

□ Input (I/P) Characteristics:

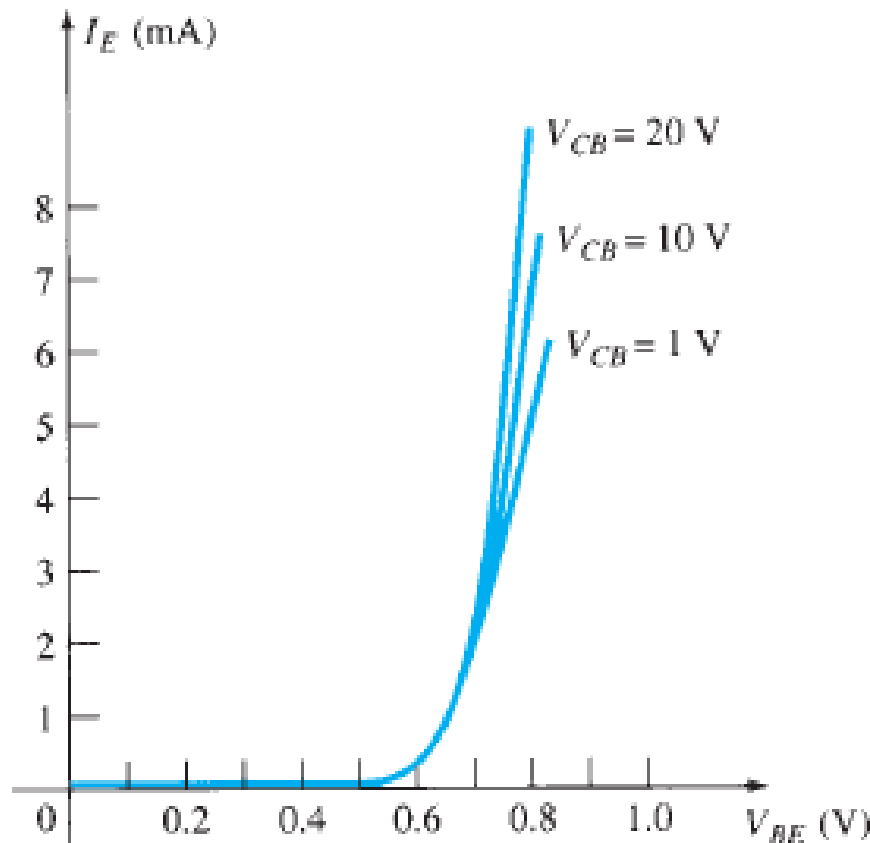


FIG. 3.7

Input or driving point characteristics for a common-base silicon transistor amplifier.

Common Base Configuration (n-p-n):

□ Output (O/P) Characteristics:


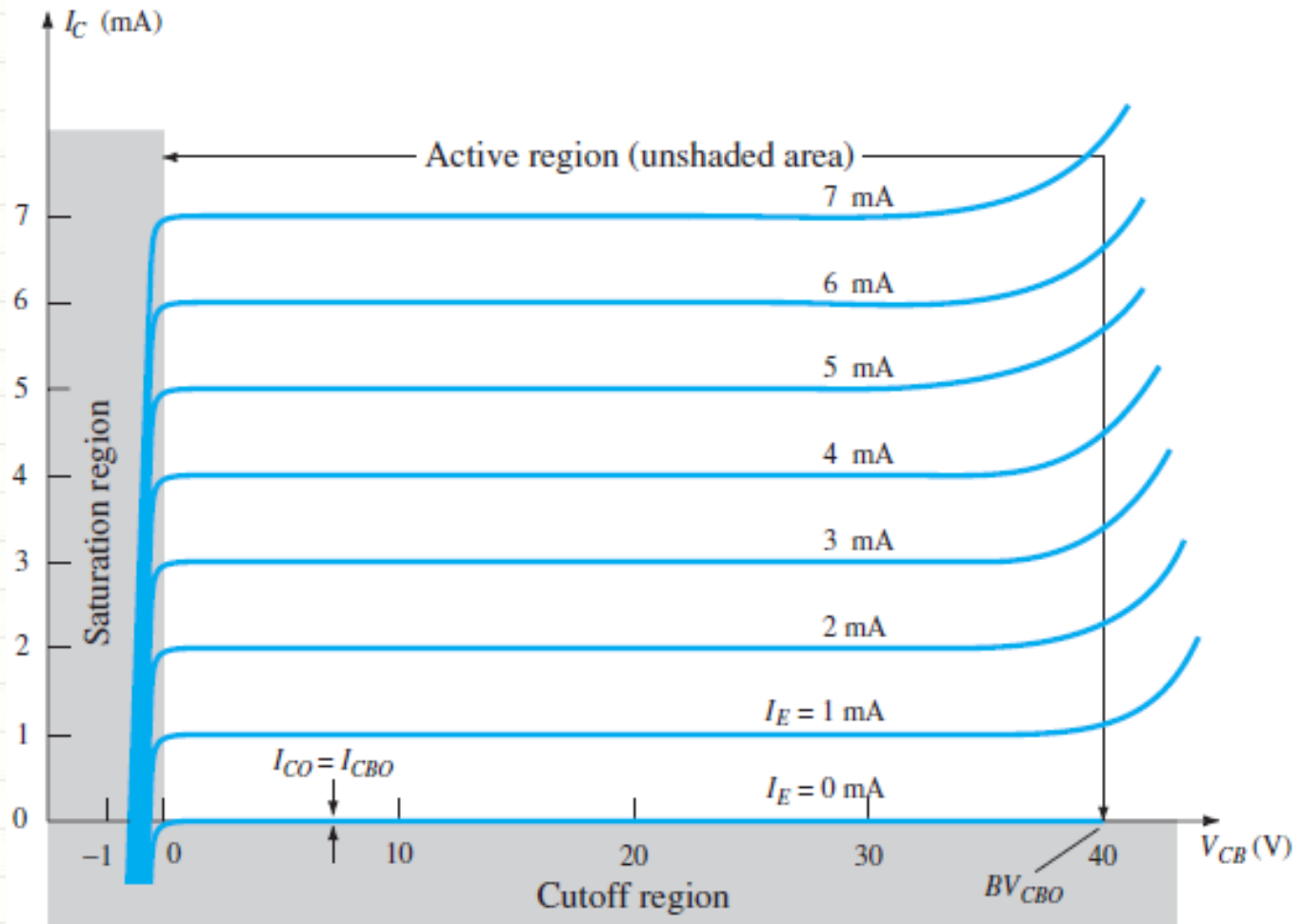


FIG. 3.8


Output or collector characteristics for a common-base transistor amplifier.

Common Emitter Configuration (n-p-n):

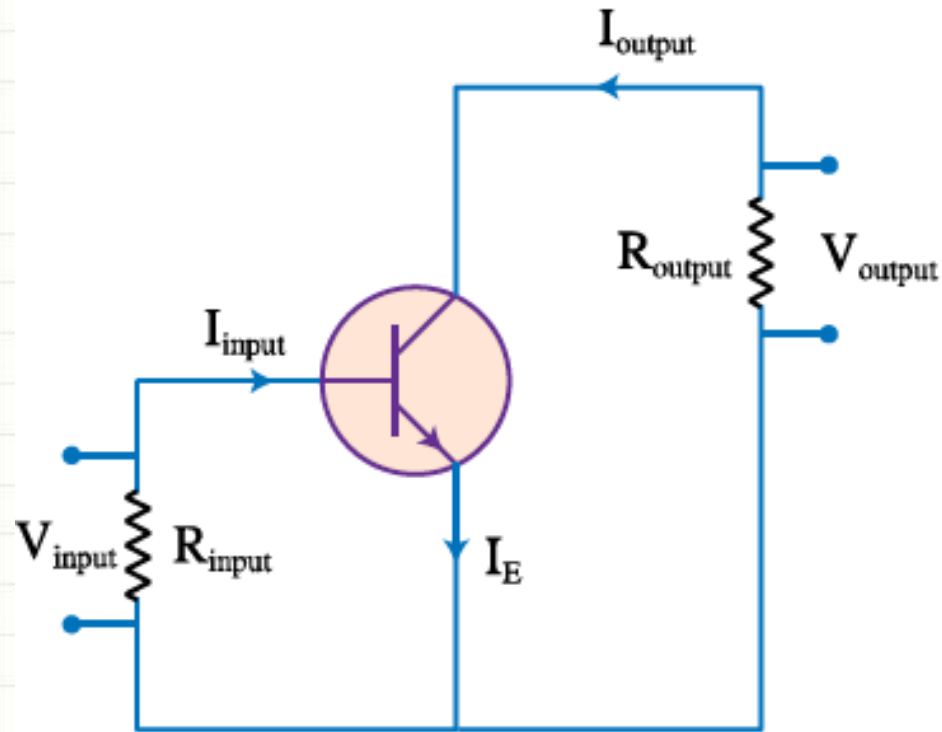


Common Emitter Configuration (n-p-n):

□ Input (I/P) Characteristics:

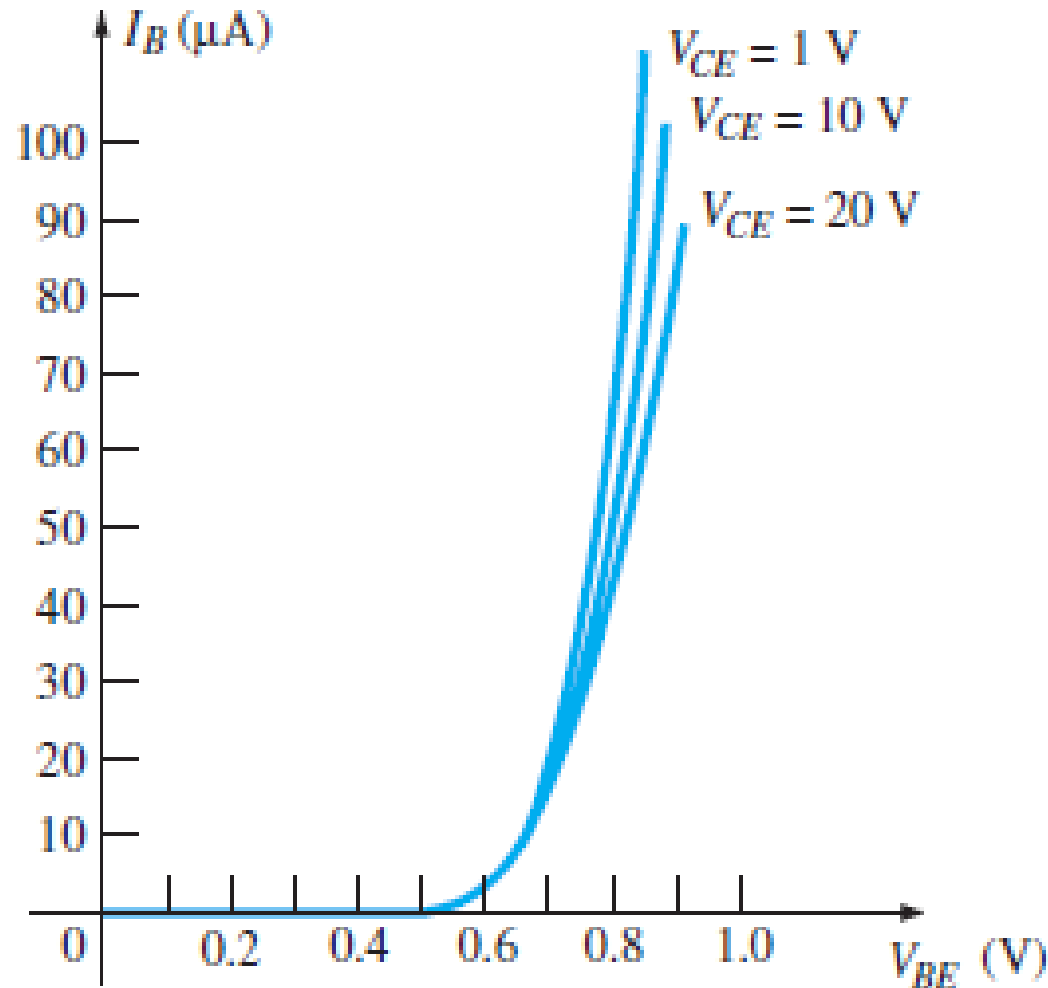

Common Emitter Configuration (n-p-n):

□ Output (O/P) Characteristics:

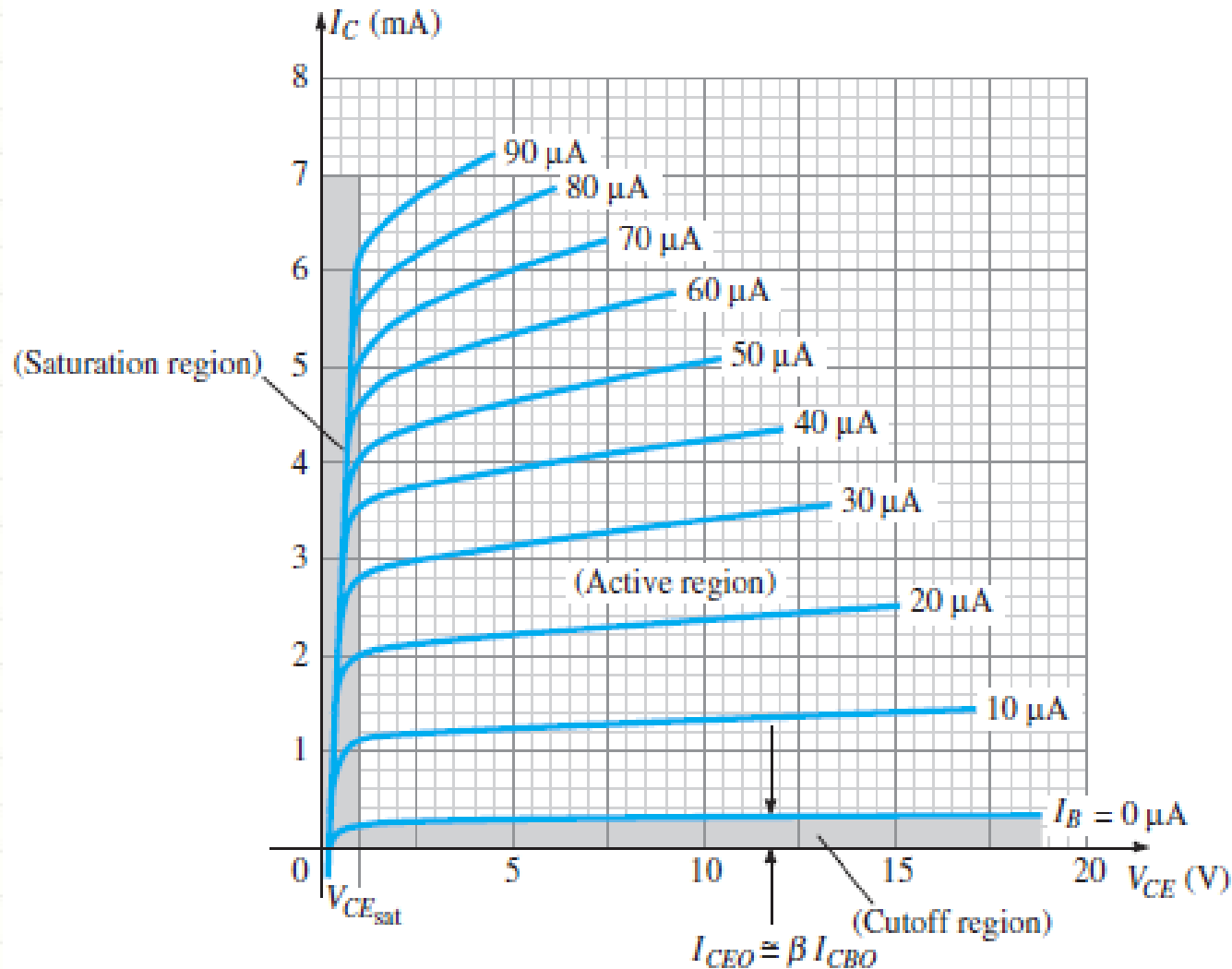



QUESTIONS?

SEE YOU IN THE NEXT CLASS

