

CSE-251

ELECTRONIC CIRCUITS


LECTURE-15

Syed Jamiul Alam
Lecturer
Department of CSE

Today's Overview:

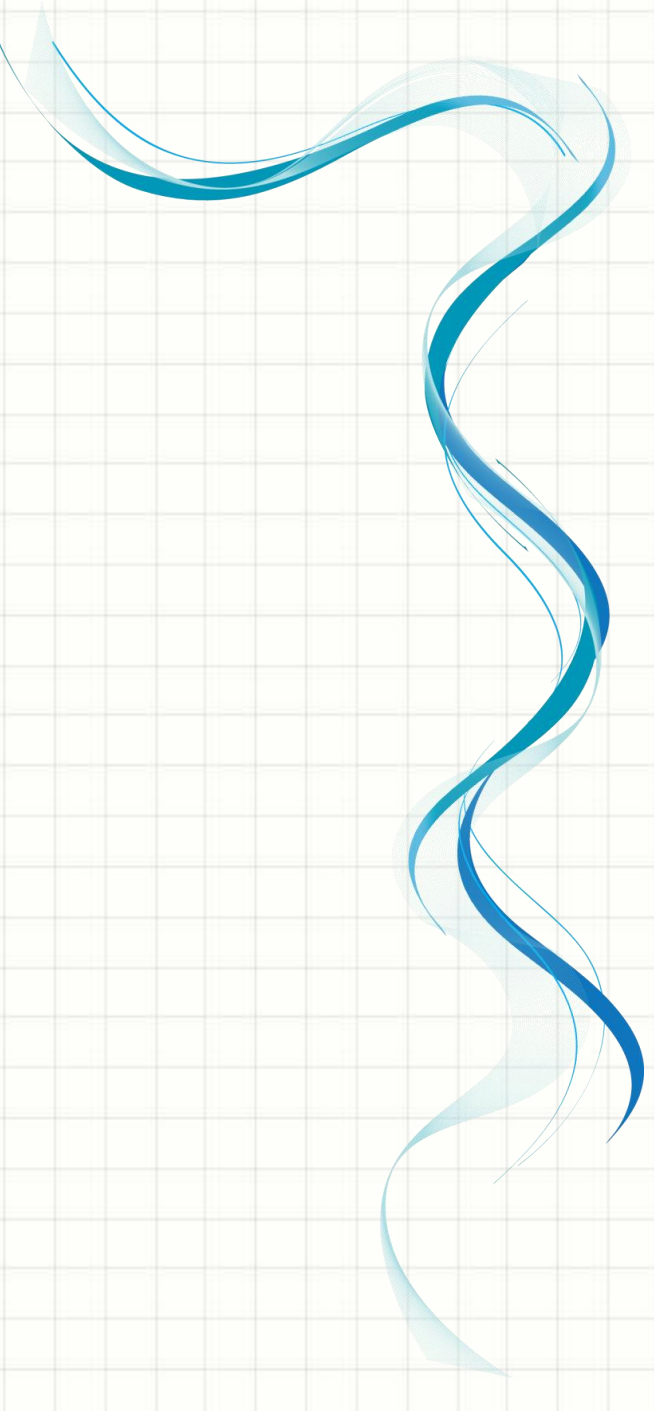
- ☐ *Subtracting Amplifier*
- ☐ *Voltage Follower*
- ☐ *Differentiator*
- ☐ *Integrator*



A decorative blue wavy line with a light blue shadow, flowing vertically on the left side of the slide.

Subtracting Amplifier


Subtracting/Difference Amplifier:

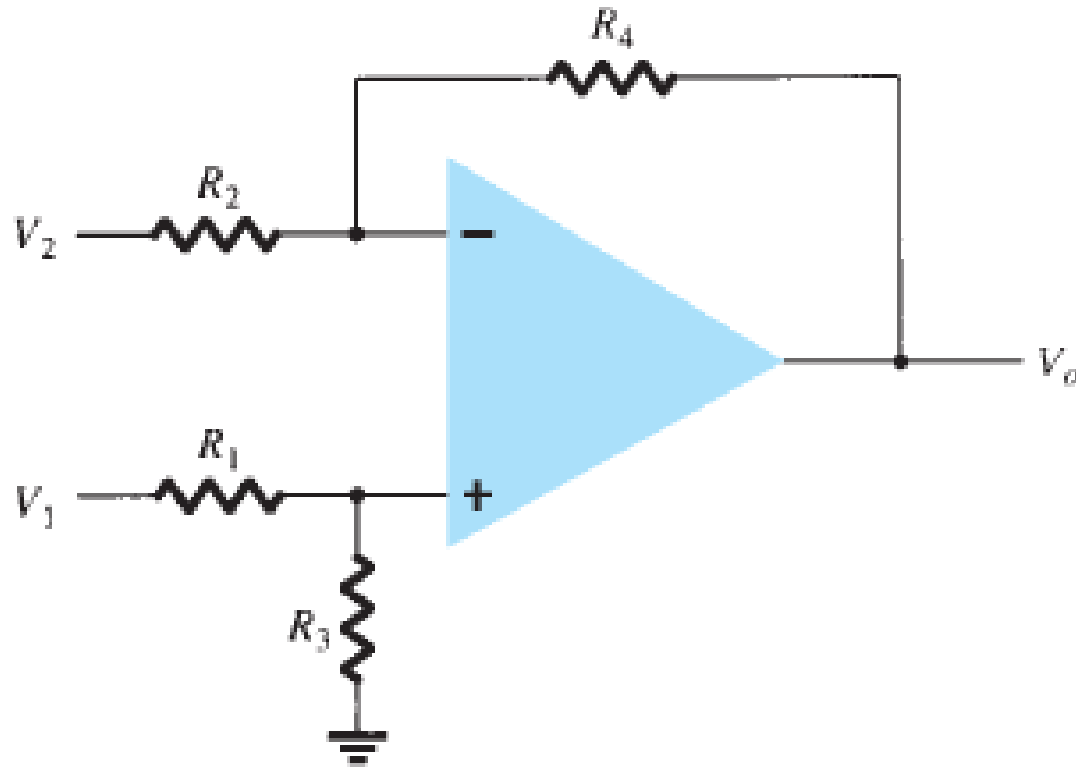

$$V_o = \frac{R_3}{R_1 + R_3} \frac{R_2 + R_4}{R_2} V_1 - \frac{R_4}{R_2} V_2$$

Problem:

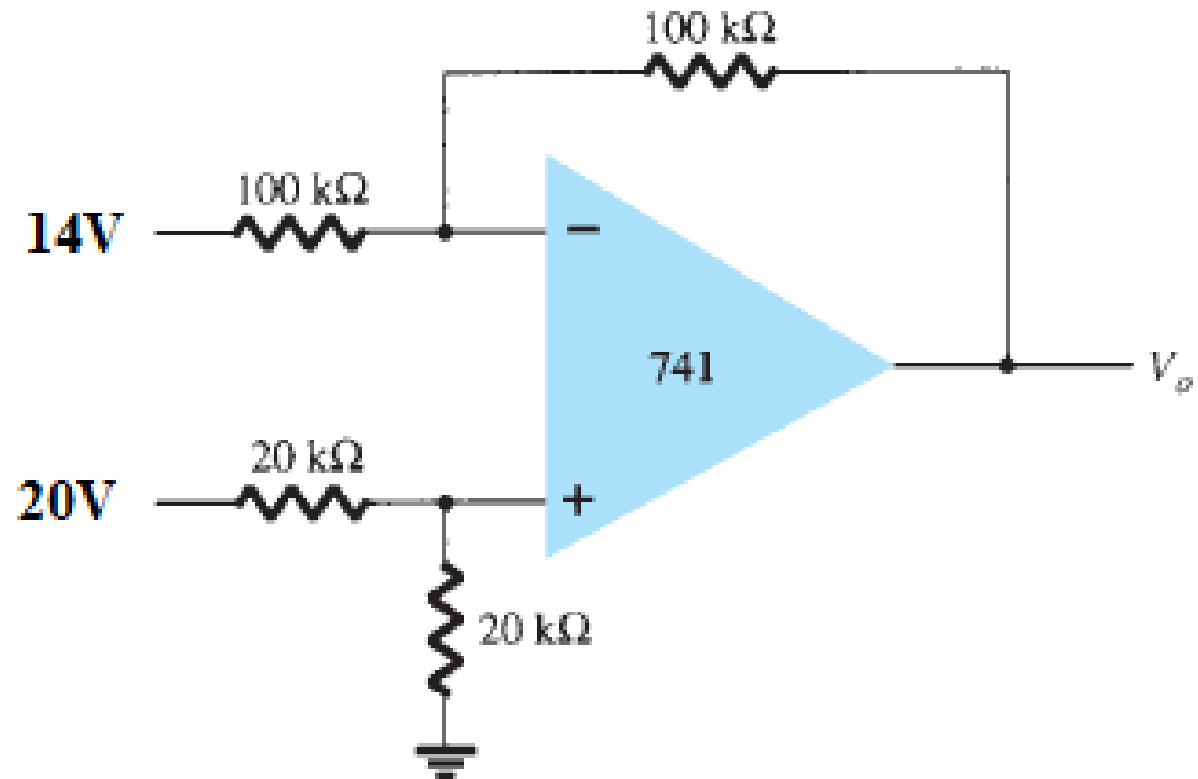EXAMPLE 11.8 Determine the output voltage for the circuit of Fig. 11.12.




Problem:

Solution: The resulting output voltage can be expressed as


$$\begin{aligned} V_o &= \left(\frac{20 \text{ k}\Omega}{20 \text{ k}\Omega + 20 \text{ k}\Omega} \right) \left(\frac{100 \text{ k}\Omega + 100 \text{ k}\Omega}{100 \text{ k}\Omega} \right) V_1 - \frac{100 \text{ k}\Omega}{100 \text{ k}\Omega} V_2 \\ &= V_1 - V_2 = 20 - 14 = 6\text{V} \end{aligned}$$

Voltage Follower

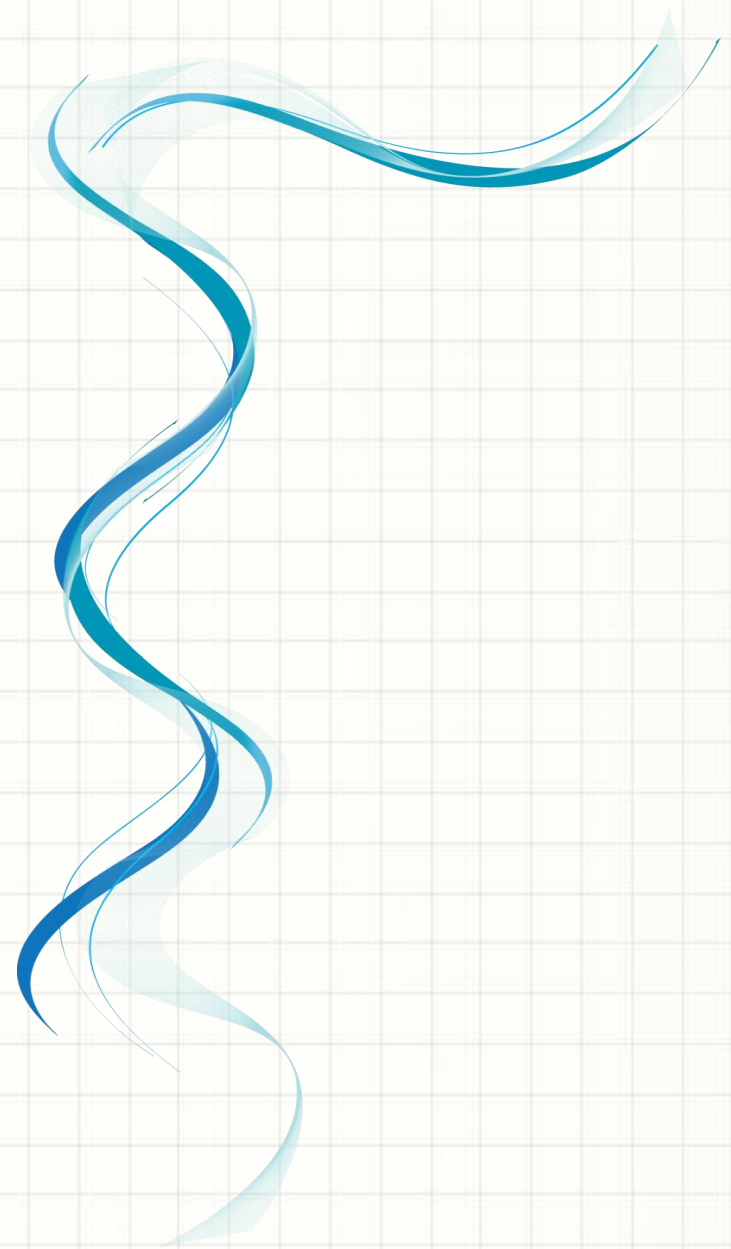

Voltage Follower/Voltage Buffer:


□ Using inverting amplifier:

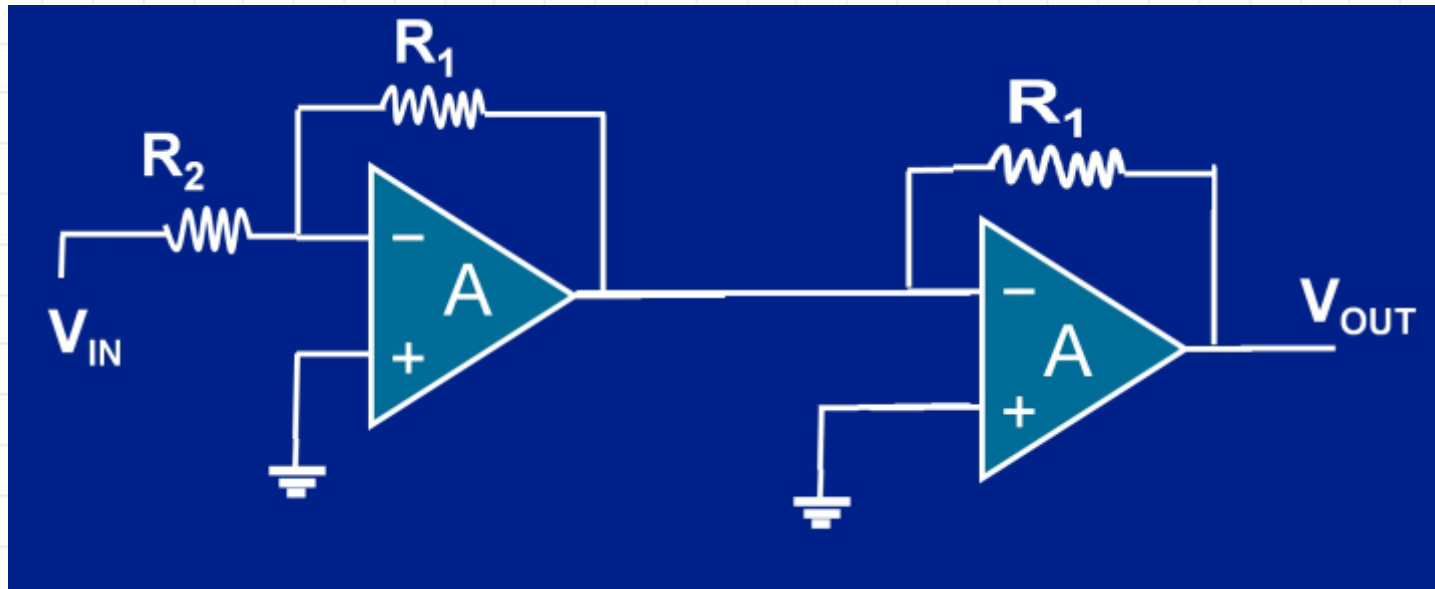


$$V_o = V_i$$

Voltage Follower/Voltage Buffer:

□ Using non-inverting amplifier:

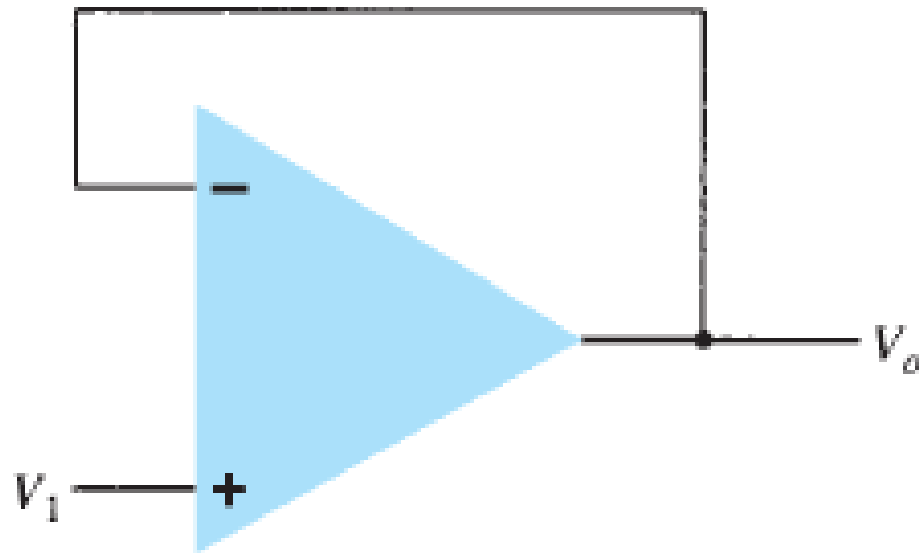

$$V_o = V_1$$

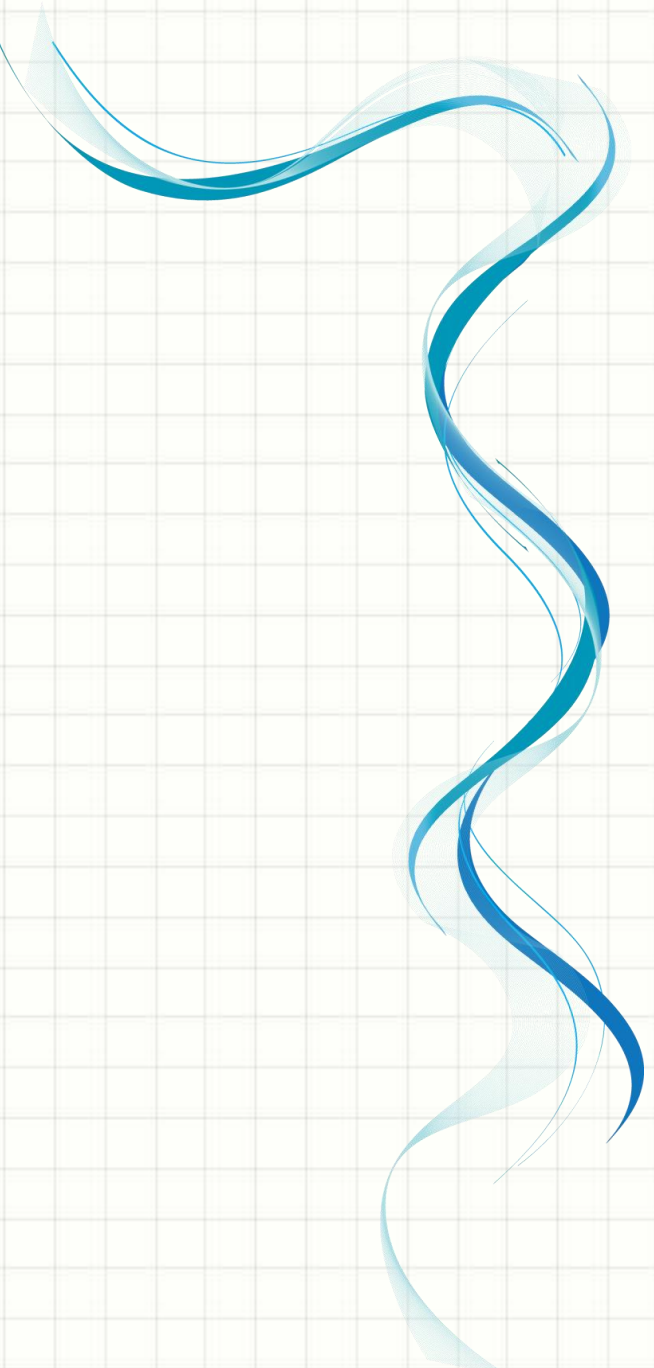A decorative blue wavy line on the left side of the slide, consisting of several overlapping, flowing curves in various shades of blue.

Differentiator

Differentiator Op-amp:

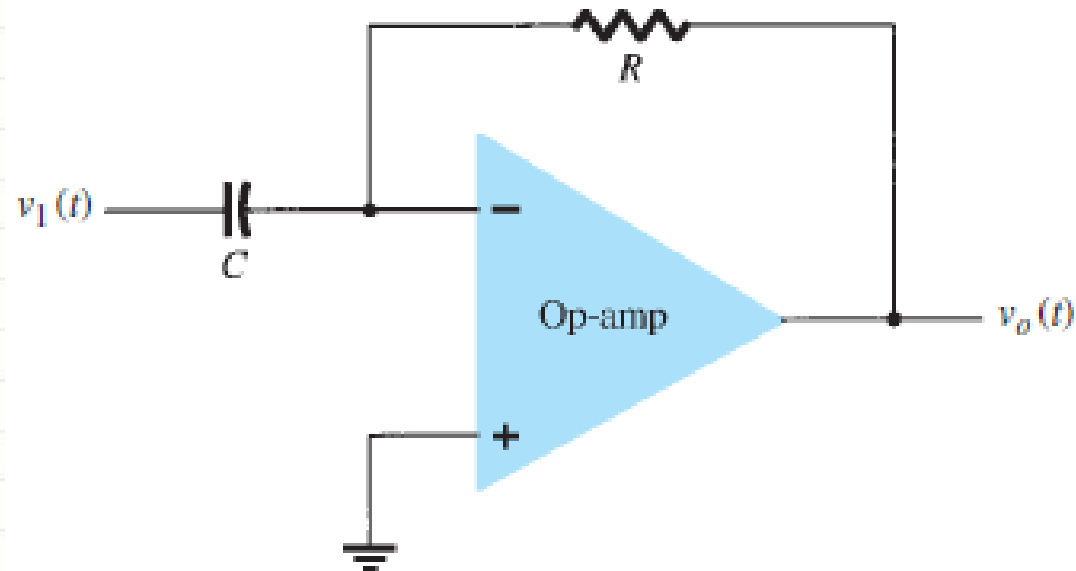



FIG. 10.41

Differentiator circuit.

$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$

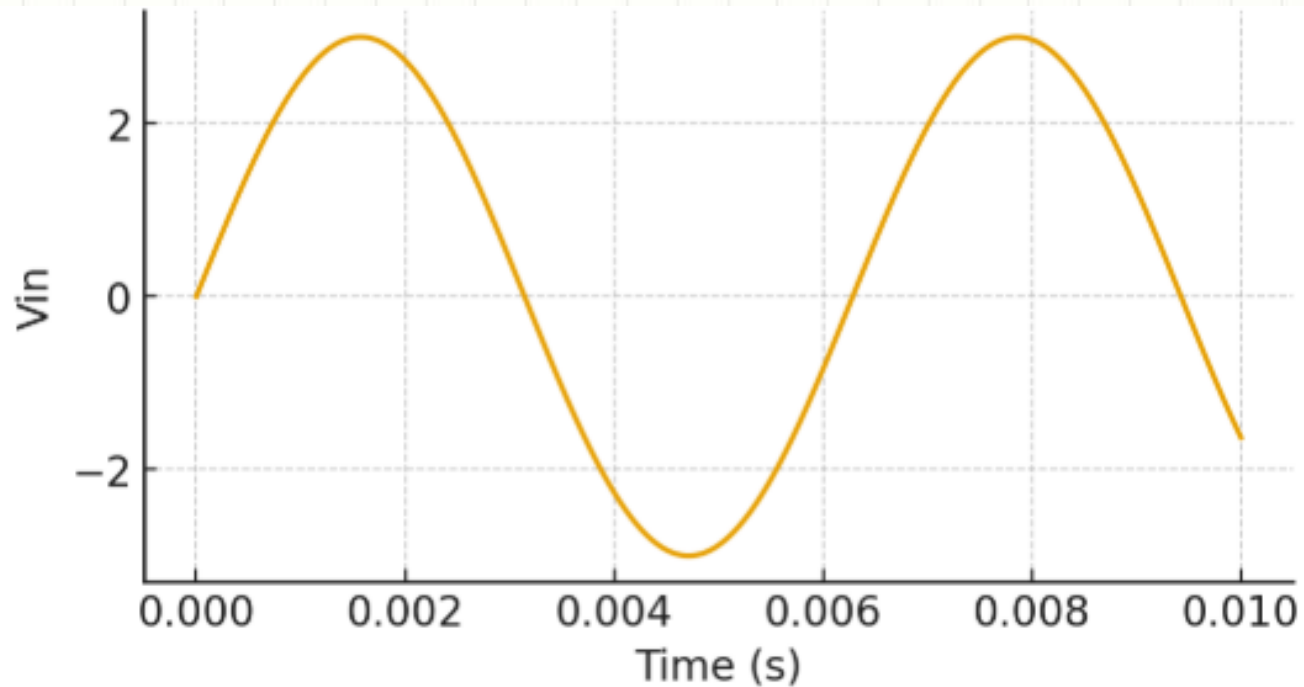Problem:

Find $v_o(t)$ for $v_{in} = 3\sin(1000t)$, $R=5k\Omega$, $C=0.02\mu F$.



Problem:


Solve:

$$\frac{d}{dt}[3 \sin(1000t)] = 3000 \cos(1000t)$$

$$RC = 5 \times 10^3 \times 2 \times 10^{-8} = 10^{-4}$$

$$v_o(t) = -10^{-4}(3000 \cos(1000t))$$

$$v_o(t) = -0.3 \cos(1000t)$$

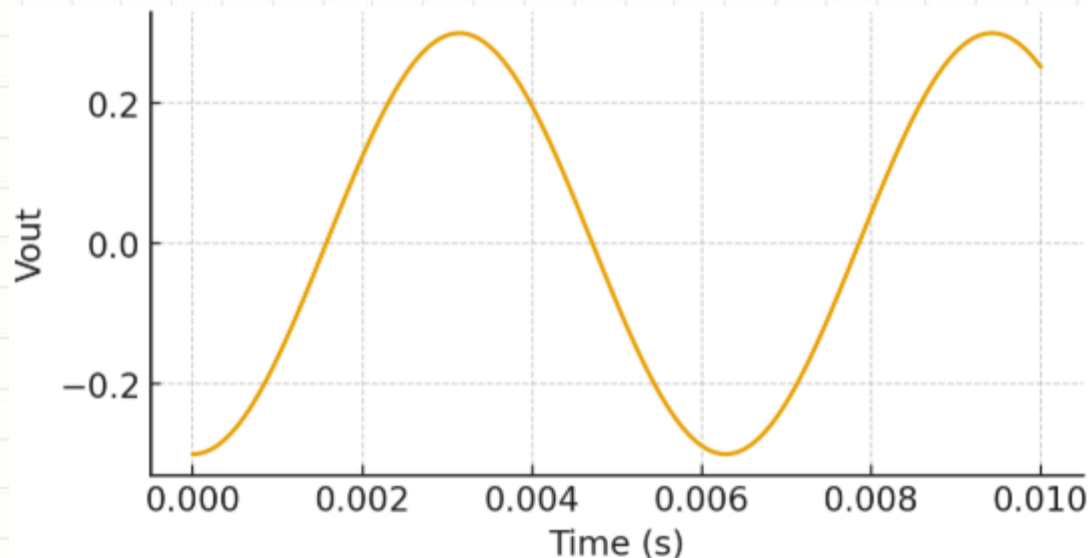

Problem:

The input is a triangular wave oscillating from 0V to 10V with a period of 2ms, $R=100\text{k}\Omega$, $C=0.1\mu\text{F}$. Find full period output of the differentiator, showing the relationship between the input and output.

Problem:

Solve:

1. Rising Edge:

The slope is:

$$\frac{dV_{in}}{dt} = \frac{10V - 0V}{2 \text{ ms}} = 5 \text{ V/ms}$$

Using the differentiator equation:

$$v_o(t) = -RC \frac{dV_{in}}{dt}$$

$$v_o(t) = -100 \times 10^3 \times 0.1 \times 10^{-6} \times 5 = -0.05 \text{ V/ms}$$

2. Falling Edge:

The slope is:



$$\frac{dV_{in}}{dt} = \frac{0V - 10V}{2 \text{ ms}} = -5 \text{ V/ms}$$

Using the same differentiator equation:

$$v_o(t) = -100 \times 10^3 \times 0.1 \times 10^{-6} \times (-5) = 0.05 \text{ V/ms}$$

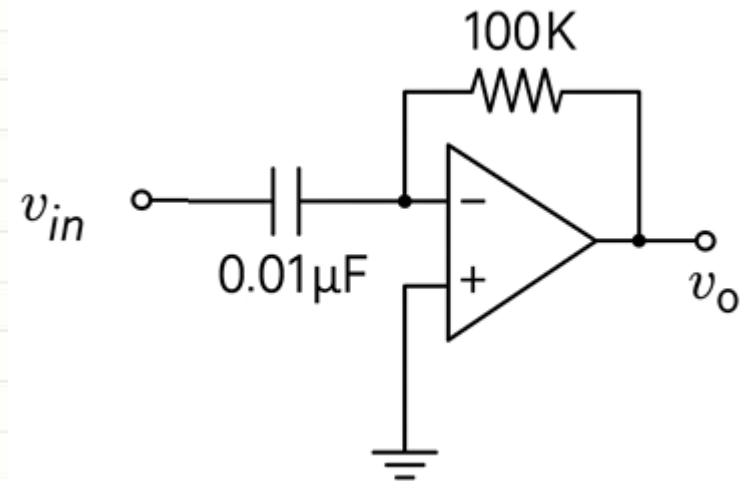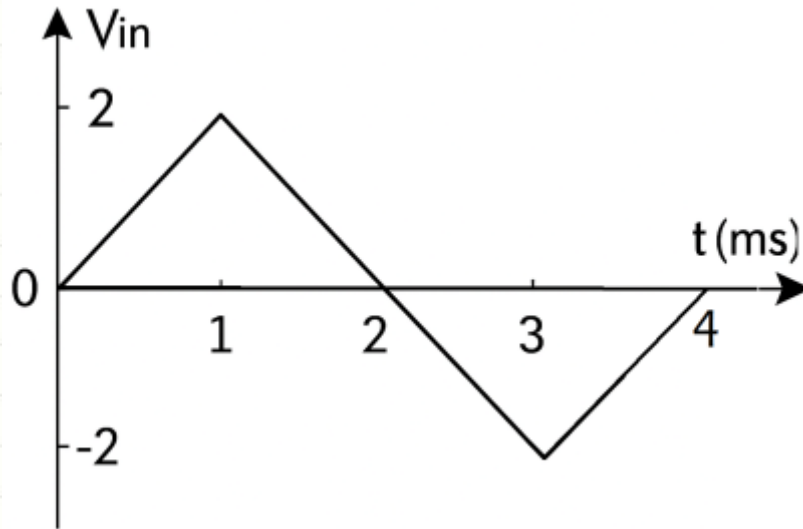
Problem:

Plot the output waveform of the given differentiator op-amp.




Problem:


Solve:

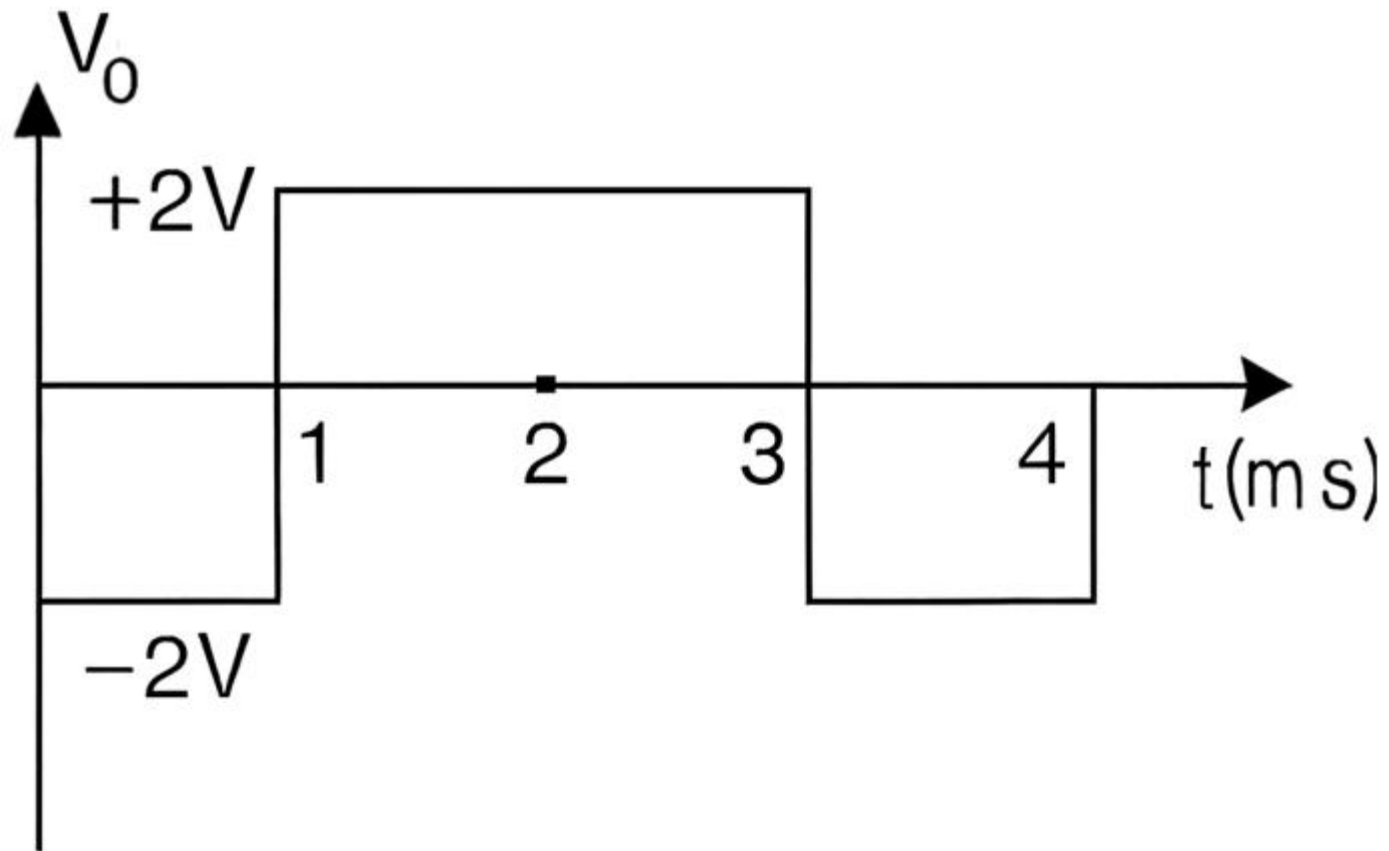

Integrator

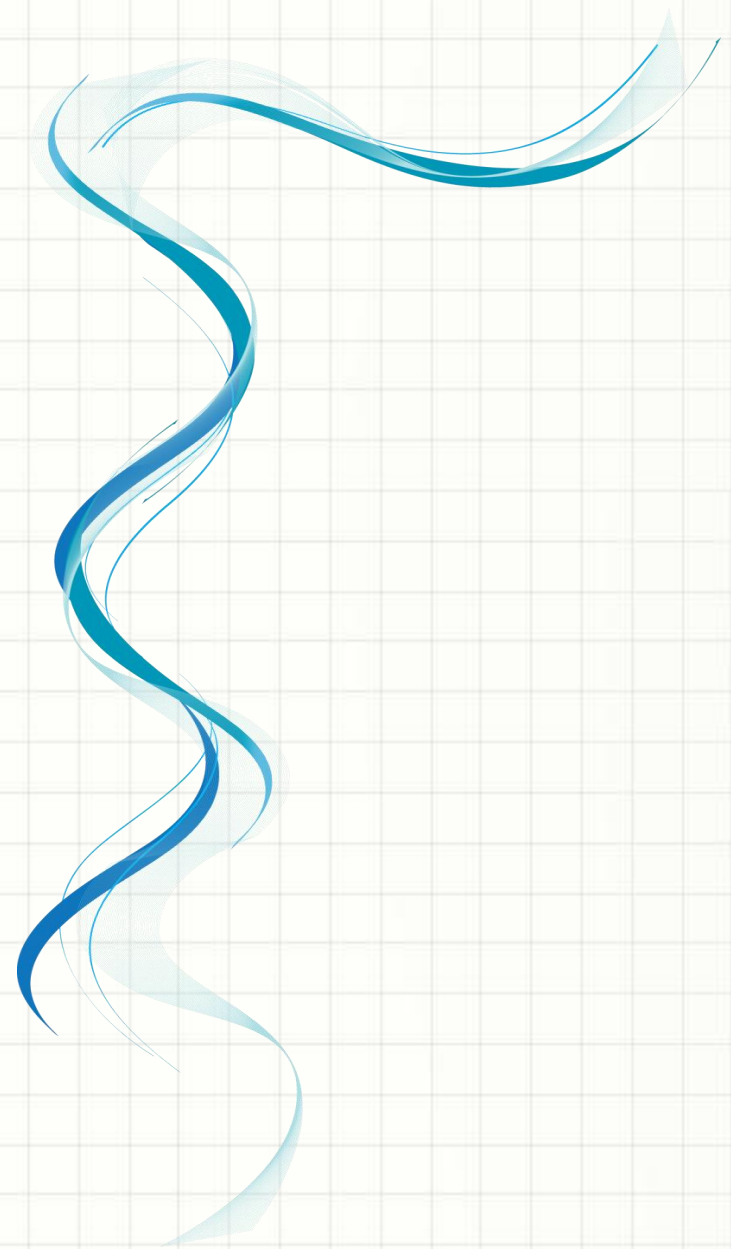


Integrator Op-amp:

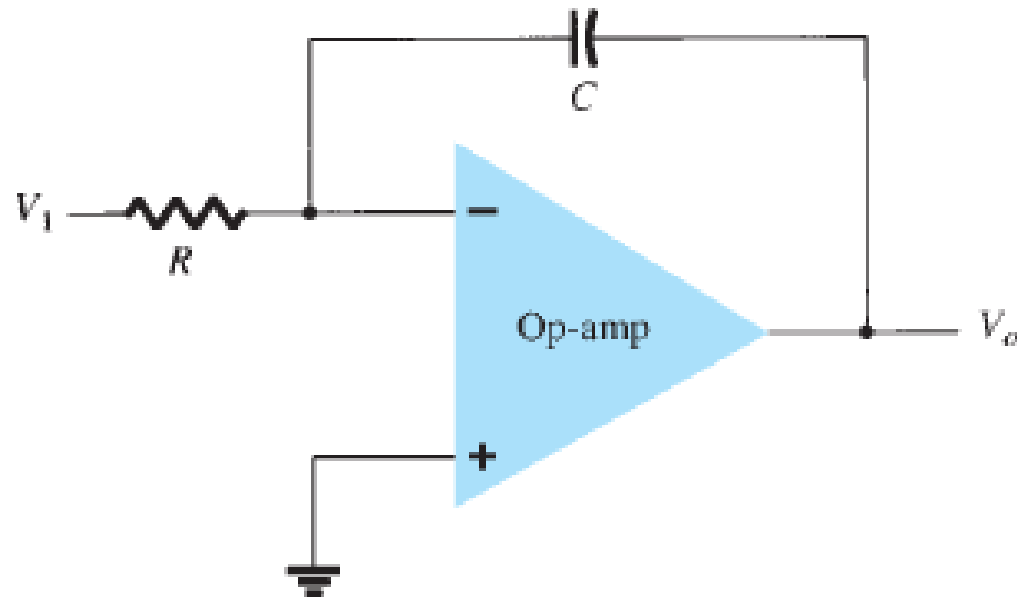

$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$

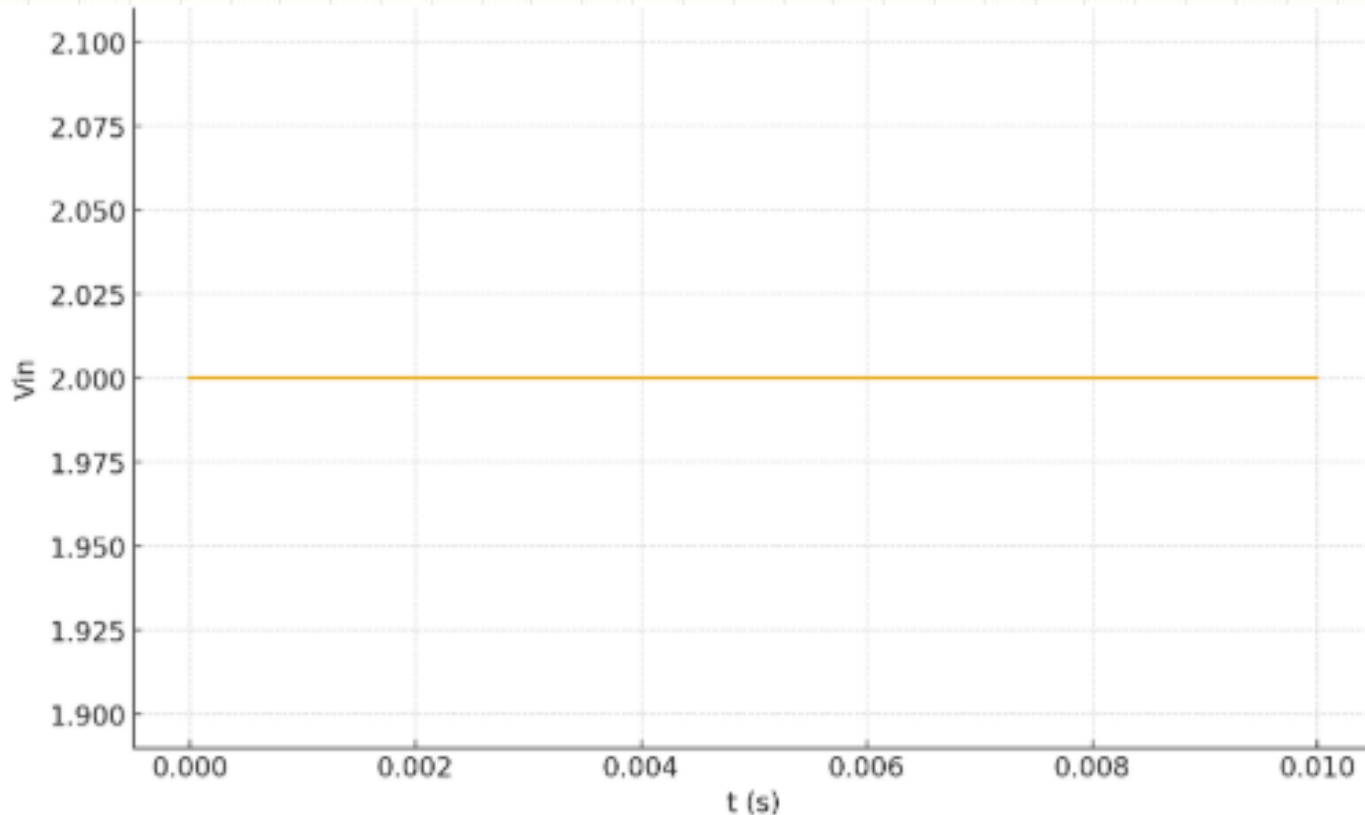Problem:

An op-amp integrator has $R=100\text{ k}\Omega$, $C=0.1\text{ }\mu\text{F}$. If the input is a constant voltage: $v_{\text{in}} = 2\text{V}$, then find the output voltage expression $v_o(t)$.




Problem:

Solve:

$$v_o(t) = -\frac{1}{RC} \int v_{in} dt$$


$$v_o(t) = -\frac{1}{100 \times 10^3 \cdot 0.1 \times 10^{-6}} (2t)$$

$$v_o(t) = -200t$$

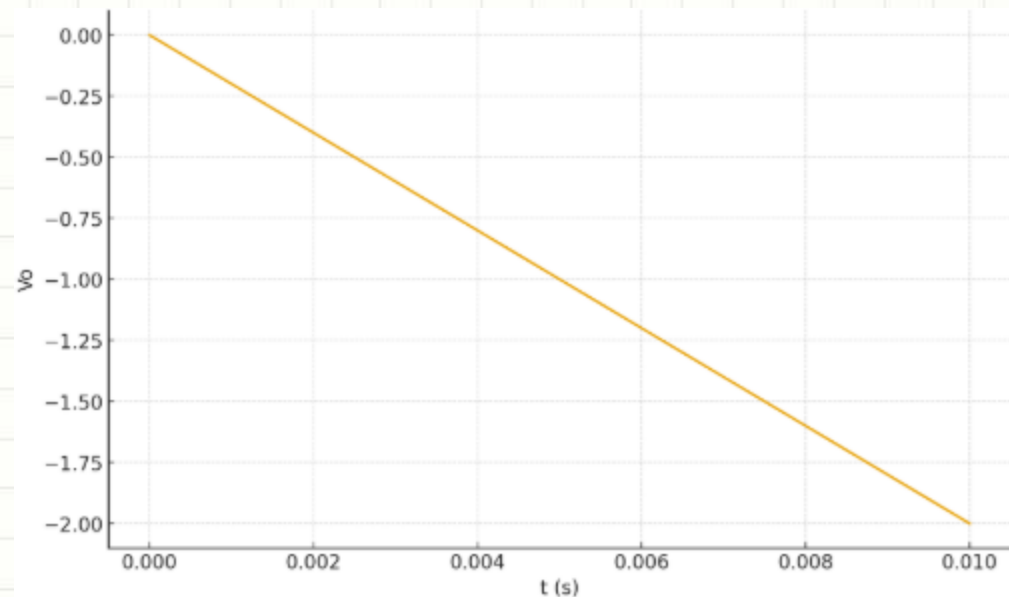

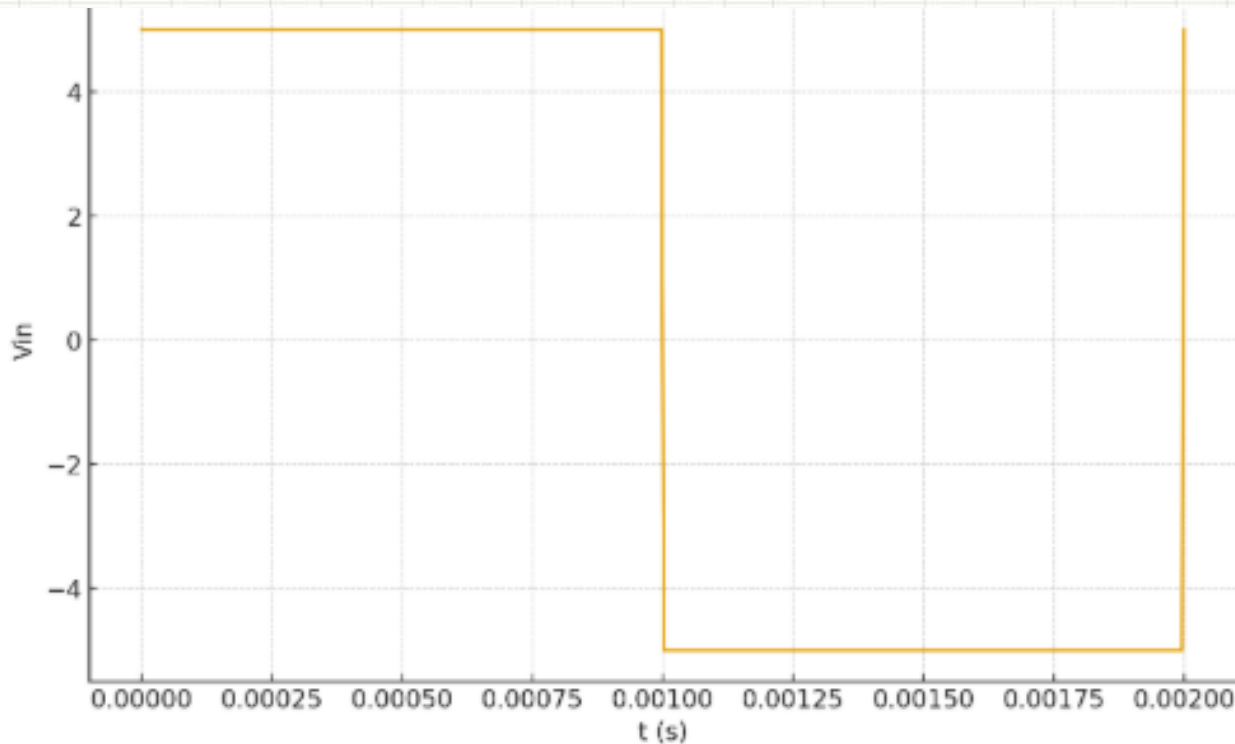Problem:

A square wave of amplitude 5V (switching between +5V and -5V) is applied to an integrator with $R=10\text{k}\Omega$, $C=0.01\mu\text{F}$. Find the slope of $v_o(t)$ in each half cycle.



Problem:

Solve:

Slope of output:

$$\frac{dv_o}{dt} = -\frac{1}{RC}v_{in}$$

$$RC = 10^4 \cdot 10^{-8} = 10^{-4}$$


Thus:

- When $v_{in} = +5$:

$$\frac{dv_o}{dt} = -\frac{5}{10^{-4}} = -5 \times 10^4 = -50,000 \text{ V/s}$$

- When $v_{in} = -5$:
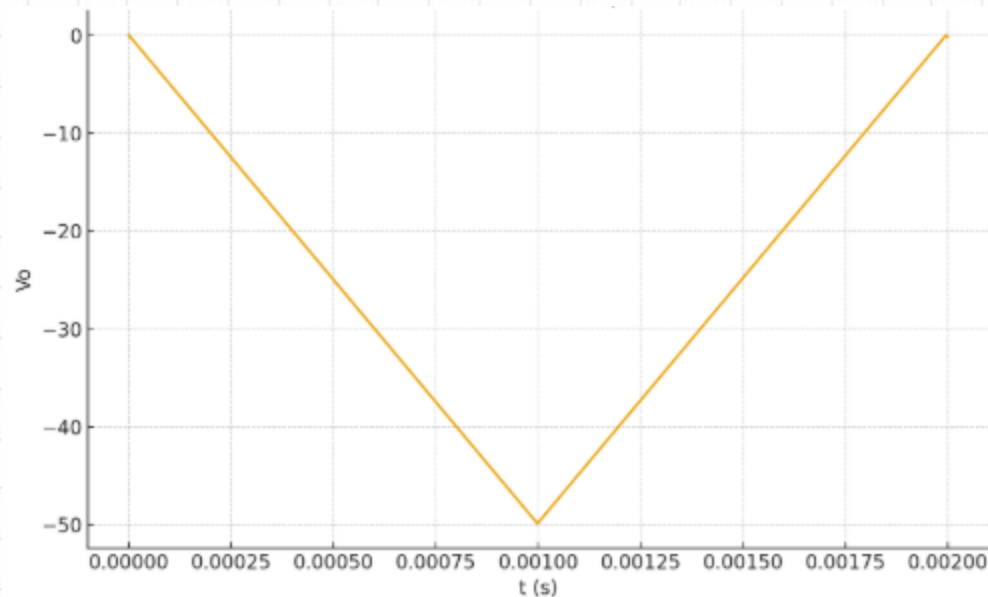
$$\frac{dv_o}{dt} = +50,000 \text{ V/s}$$



Problem:

Find $v_o(t)$ for $v_{in} = 2\sin(1000t)$ and $RC=1$.

Problem:

Solve:

$$\begin{aligned}v_o(t) &= -\frac{1}{RC} \int 2 \sin(1000t) dt \\&= -2 \left(\frac{-\cos(1000t)}{1000} \right) \\&= \frac{2}{1000} \cos(1000t) \\&= 0.002 \cos(1000t)\end{aligned}$$



QUESTIONS?

SEE YOU IN THE NEXT CLASS

