




EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Mid Term I Examination, Fall 2021 Semester


Course: CSE 209 Electrical Circuits, Section-3
Instructor: Musharrat Khan, Senior Lecturer, CSE Department
Full Marks: 40 (20 will be counted for final grading)
Time: 1 Hour and 25 Minutes (Including Submission)

Note: There are FIVE questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

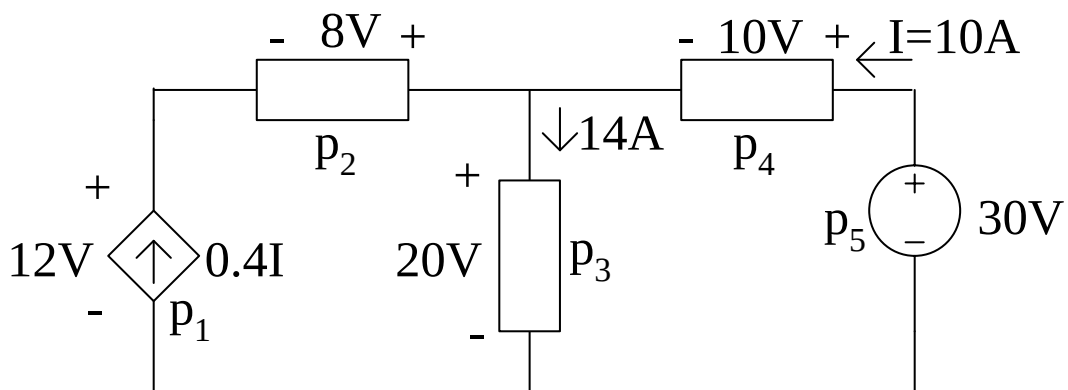
1. **Compute** the power absorbed or supplied by each component of the following circuit. [CO1,C2, Mark:6]



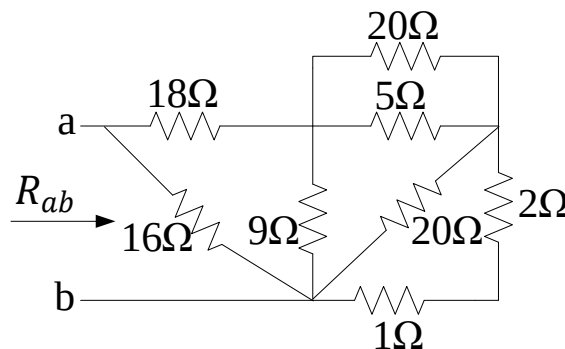2. **Find** equivalent resistance R_{ab} for the following circuit. [CO1,C2, Mark: 6]




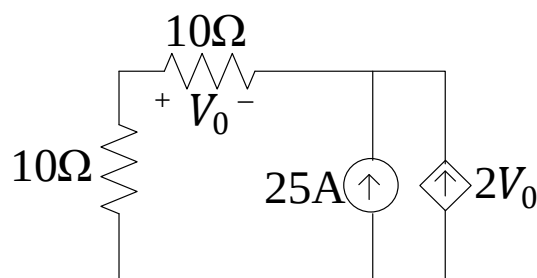3. **Calculate** V_0 in the following circuit and the power absorbed by the dependent source. [CO1,C3, Mark: 8]



4. Calculate I in the following circuit using delta-wye transformation.

[CO1,C3,
Mark: 8]

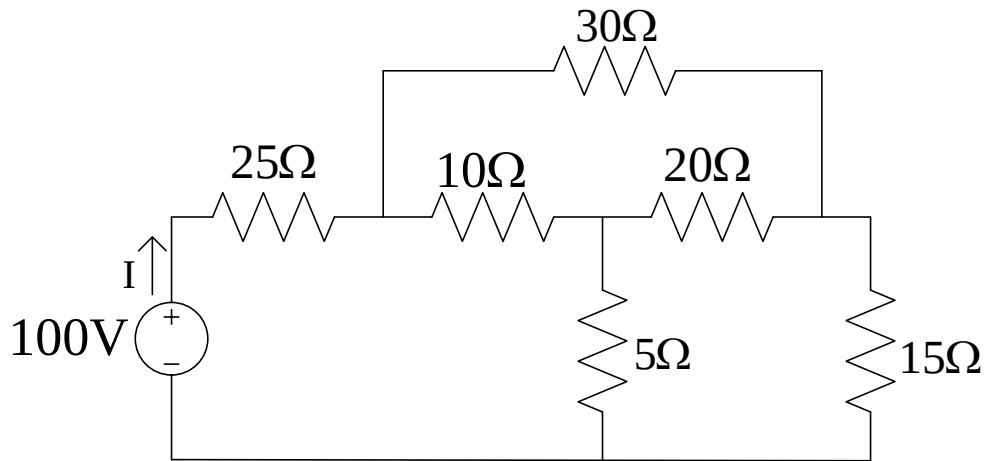

5. Determine the non-reference node voltage for calculating i and then from that non-reference node voltage calculate i in the following circuit.

[CO2,C4,
Mark:12]

