



EAST WEST UNIVERSITY

Department of Computer Science and Engineering


Fall 2021 Semester

CSE209 Electrical Circuits, Section-3, Class Test-1

Marks:10

Time: 20 minutes

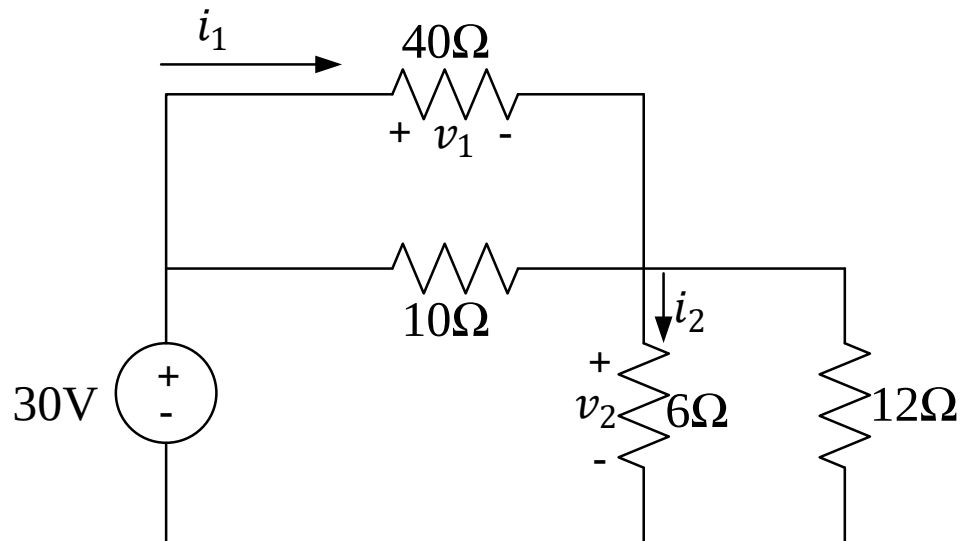1. Find v_1 and v_2 in the following circuit. Also calculate i_1 and i_2 in the following circuit. [8]



2. Transform wye to delta. [2]

