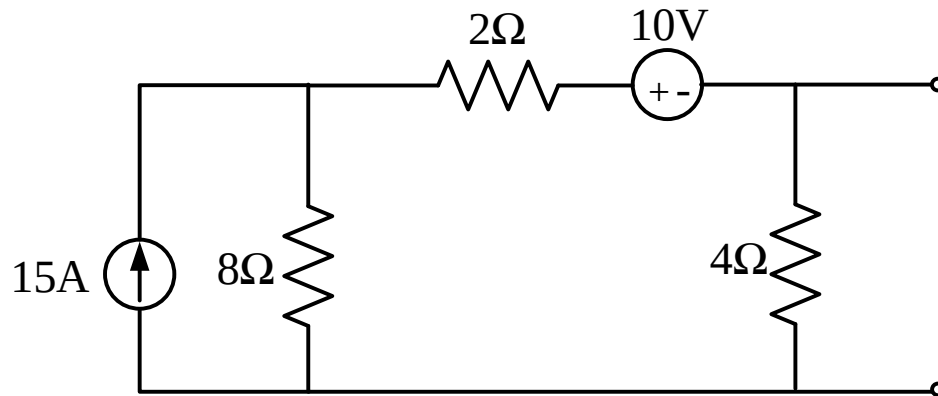




EAST WEST UNIVERSITY
Department of Computer Science and Engineering
Fall 2021 Semester
CSE209 Electrical Circuits, Section-3, Class Test-2
Marks:10
Time: 25 minutes

1. Determine the Thevenin's equivalent circuit for the following circuit. [5]



2. Using source transformation, find v in the following circuit. [5]

