



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
Fall 2021 Semester
CSE209 Electrical Circuits, Section-3, Class Test-3
Marks:10
Time: 20 minutes

1. Using superposition theorem, find v_x and i_x in the following circuit.

