



# East West University

**Department of Computer Science and Engineering**

**Semester : spring 2021**

**Course Title:** Electrical Circuits

**Course Code:** CSE 209

**Section:** 03

**Experiment No:** 02

**Experiment Title:** Series – Parallel DC Circuit and Verification of Kirchhoff's Laws

**Student Name:** Md. Rakibur Rahman

**ID:** 2019-3-60-113


**Date of Performance:** 22.03.2021

**Date of Submission:** 28.03.2021

## Objectives:

1. To learn analysis of dc series-parallel circuit.
2. To verify Kirchhoff's voltage law (KVL).
3. To verify Kirchhoff's current law (KCL).

## Circuit Diagram:

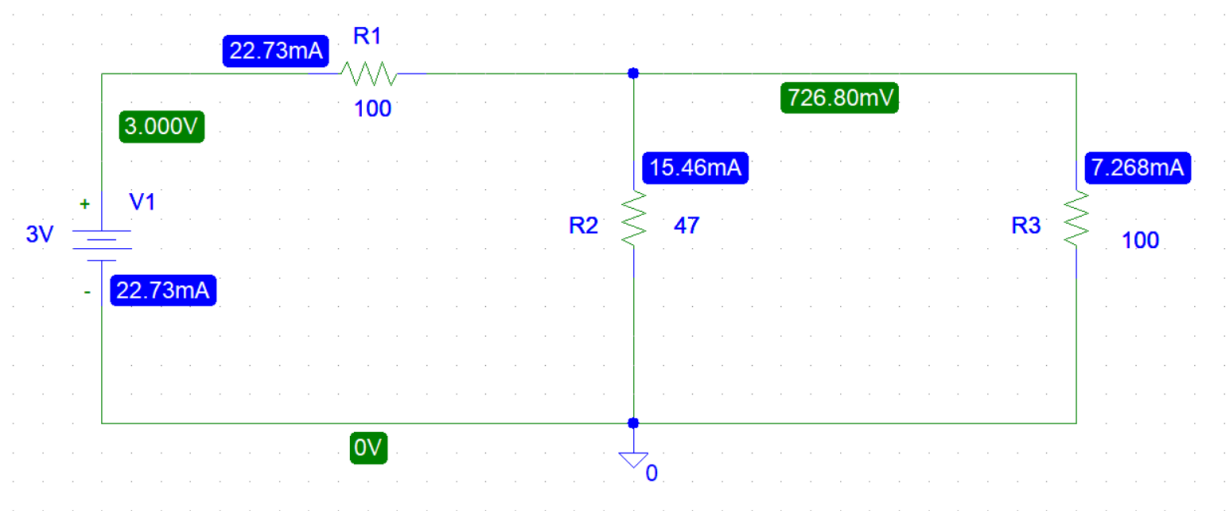

## Experimental Datasheet:

| Measured Value of E(V) | Measured Value of V <sub>1</sub> (V) | Measured Value of V <sub>2</sub> (V) | Measured Value of V <sub>3</sub> (V) | Measured Value of I <sub>1</sub> (mA) | Measured Value of I <sub>2</sub> (mA) | Measured Value of I <sub>3</sub> (mA) | Measured Value of Resistance( $\Omega$ )                                                    |
|------------------------|--------------------------------------|--------------------------------------|--------------------------------------|---------------------------------------|---------------------------------------|---------------------------------------|---------------------------------------------------------------------------------------------|
| 3                      | 3                                    | 0.7268                               | 0.7268                               | 22.73                                 | 15.46                                 | 7.268                                 | R <sub>1</sub> =100 $\Omega$<br>R <sub>2</sub> =47 $\Omega$<br>R <sub>3</sub> =100 $\Omega$ |

### Answers to the post lab report questions:

1. Here ,  $R_2$  and  $R_3$  are parallel,

So, Equivalent resistance,  $R_p = \frac{47 \times 100}{47 + 100} = 31.973 \Omega$

Applying voltage divider rule,

$$\begin{aligned} V_1 &= \frac{E}{R_1 + R_p} \times R_1 \\ &= \frac{3}{100 + 31.973} \times 100 \\ &= 2.273V \end{aligned}$$

$$\begin{aligned} V_2 &= \frac{E}{R_1 + R_p} \times R_p \\ &= \frac{3}{100 + 31.973} \times 31.973 \\ &= 0.727V \end{aligned}$$

Here ,  $V_2$  and  $V_3$  are parallel.

So ,  $V_2 = V_3 = 0.727V$  . Because the voltage is equal in Parallel Circuit .

From Ohm's Law,

$$\begin{aligned} I_1 &= \frac{E}{R_1 + R_p} \\ &= \frac{3}{100 + 31.973} \\ &= 0.02273A \\ &= 22.73mA \end{aligned}$$

Applying current divider rule,

$$I_2 = \frac{I_1}{R_2 + R_3} \times R_3$$

$$= \frac{22.73}{47 + 100} \times 100$$

$$= 15.463\text{mA}$$

$$I_3 = \frac{I_1}{R_2 + R_3} \times R_2$$

$$= \frac{22.73}{47 + 100} \times 47$$

$$= 7.267\text{mA}$$

Comparing the theoretically calculated values with the simulated values from PSpice.

|         | Calculated value                     | Measured value          |
|---------|--------------------------------------|-------------------------|
| Current | $I_1 = 22.73\text{mA}$               | $I_1 = 22.73\text{mA}$  |
|         | $I_2 = 15.463\text{mA}$              | $I_2 = 15.46\text{mA}$  |
|         | $I_3 = 7.267\text{mA}$               | $I_3 = 7.268\text{mA}$  |
| Voltage | $V_1 = 2.273\text{V}$                | $V_1 = 3\text{V}$       |
|         | $V_2 = 0.727\text{V} = 727\text{mV}$ | $V_2 = 726.80\text{mV}$ |
|         | $V_3 = 0.727\text{V} = 727\text{mV}$ | $V_3 = 726.80\text{mV}$ |

The experimental values of the voltages and the currents are slightly different from the theoretical values.

2. (i) From the calculated values we get,

$$V_2 = V_3 = 0.727\text{V}$$

Here, both  $V_2$  and  $V_3$  are parallel in the circuit so the voltage are same.

(ii) From the calculated values we get,

$$V_1 = 2.273V$$

$$V_2 = 0.727V$$

Applying KVL,

$$V_1 + V_2 = (2.273 + 0.727)V$$

$$= 3V$$

$$= E$$

(iii) From the calculated values we get,

$$I_1 = 22.73mA$$

$$I_2 = 15.463mA$$

$$I_3 = 7.267mA$$

Applying KCL,

$$I_2 + I_3 = (15.463 + 7.267)mA$$

$$= 22.73mA$$

$$= I_1$$

**Conclusion:**

From the experiment we learnt about the application Ohm's Law, Kirchhoff's Voltage Law(KVL) and Kirchhoff's Current Law(KCL).