
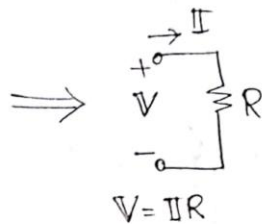


9.1 Phasor Relationships for Circuit Elements

Impedance Unit $\rightarrow \Omega$



Resistor:

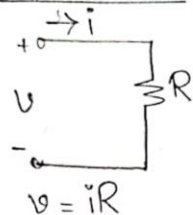

$$Z_R = \frac{V}{I} = R$$

$$Z_R = R \angle 0^\circ \text{ Impedance of Resistance}$$

Inductor:

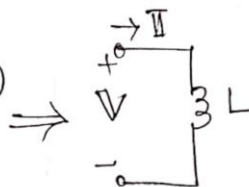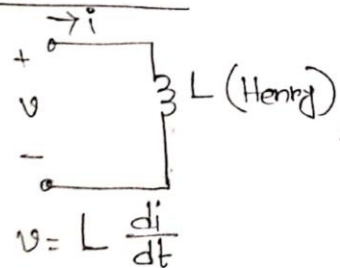

$$V = L j\omega I$$


$$V = j\omega L I$$

$$Z_L = \frac{V}{I} = j\omega L$$

$$Z_L = \omega L \angle 90^\circ$$


Impedance of Inductance

Capacitor:

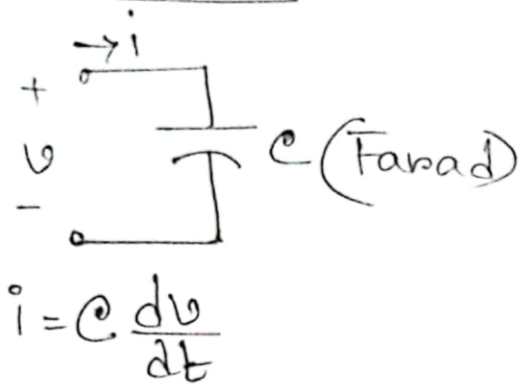

$$i = C \frac{dv}{dt}$$

$\Rightarrow$

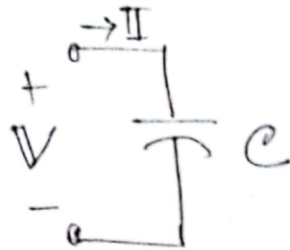

$$I = C j\omega V$$

$$V = \frac{I}{j\omega C}$$

$$Z_C = \frac{V}{I} = \frac{1}{j\omega C}$$

$$Z_C = \frac{-j}{\omega C}$$

$$Z_C = \frac{1}{\omega C} \angle -90^\circ$$

Impedance of Capacitance

Example 9.8

$$v = 12 \cos(60t + 45^\circ) \text{ V}$$

$$L = 0.1 \text{ H}$$

$$i = ?$$

$$V = 12 \angle 45^\circ \text{ V}$$

$$Z_L = j\omega L = j \times 60 \times 0.1 = j6 \, \Omega$$

$$Z_L = \frac{V}{I}$$

$$I = \frac{V}{Z_L} = \frac{12 \angle 45^\circ}{j6} = 2 \angle -45^\circ \text{ A}$$

$$i = 2 \cos(60t - 45^\circ) \text{ A}$$

Practice Problem 9.8

$$v = 10 \cos(100t + 30^\circ) \text{ V}$$

$$C = 50 \, \mu\text{F} = 50 \times 10^{-6} \text{ F}$$

$$i = ?$$

$$V = 10 \angle 30^\circ \text{ V}$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 100 \times 50 \times 10^{-6}} = \frac{1}{j5 \times 10^{-3}} \, \Omega$$

$$I = \frac{V}{Z_C} = 10 \angle 30^\circ \times j5 \times 10^{-3} = 50 \angle 120^\circ \text{ mA}$$



$$i = 50 \cos(100t + 120^\circ) \text{ mA}$$

$$Z_R = R \angle 0^\circ \Omega$$

$$Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C}$$
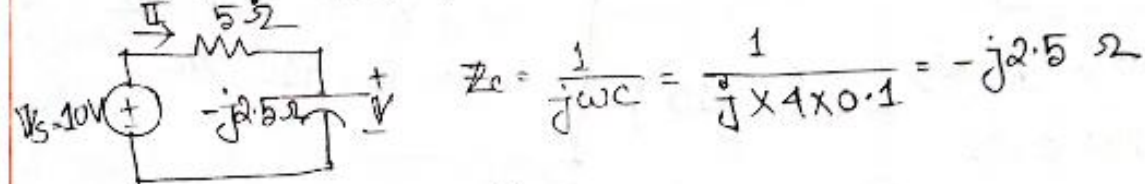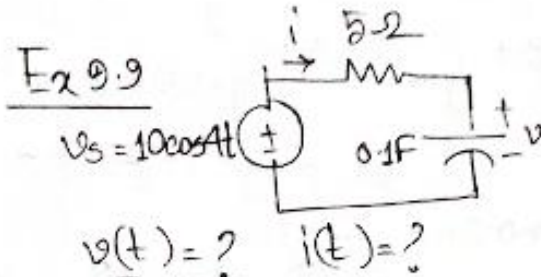
$$\begin{aligned}\sin(\omega t \pm 180^\circ) &= -\sin \omega t \\ \cos(\omega t \pm 180^\circ) &= -\cos \omega t \\ \sin(\omega t \pm 90^\circ) &= \pm \cos \omega t \\ \cos(\omega t \pm 90^\circ) &= \mp \sin \omega t\end{aligned}$$



$$Z = Z_R + Z_C = (5 - j2.5) \Omega$$

$$I = \frac{V_s}{Z} = \frac{10 \angle 0^\circ}{5 - j2.5} = (1.6 + j0.8) \text{ A} = 1.789 \angle 26.565^\circ \text{ A}$$


$$i(t) = 1.789 \cos(4t + 26.565^\circ) \text{ A}$$

$$V = I Z_C = 1.789 \angle 26.565^\circ \times (-j2.5) = 4.473 \angle -63.435^\circ \text{ V}$$


$$v(t) = 4.473 \cos(4t - 63.435^\circ) \text{ V}$$

P.P. 9.9

Ex 9.10

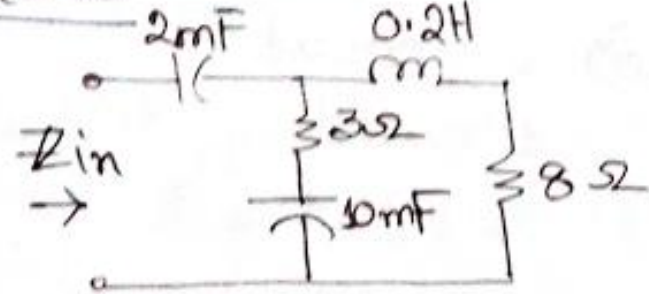

Given, $\omega = 50 \text{ rad/s}$

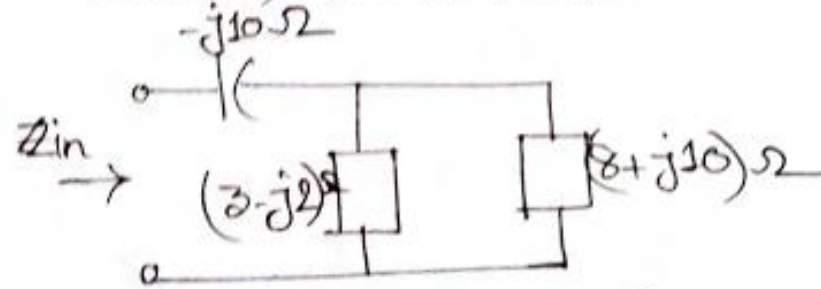

$$\begin{aligned}
 Z_{in} &= \frac{(8+j10) \times (3-j2)}{8+j10+3-j2} + (-j10) \\
 &= \frac{(8+j10) \times (3-j2)}{11+j8} - j10 \\
 &= (3.22 - j11.07) \Omega
 \end{aligned}$$

Ex 9.11, P.P. 9.11 $\Rightarrow$ Do Practice

2mF:

$$\begin{aligned}
 Z_c &= \frac{1}{j\omega c} = \frac{1}{j \times 50 \times 2 \times 10^{-3}} \\
 &= -j10 \Omega
 \end{aligned}$$

$$\begin{aligned}
 3 + \frac{1}{j\omega c} &= 3 + \frac{1}{j \times 50 \times 10 \times 10^{-3}} \\
 &= (3-j2) \Omega
 \end{aligned}$$

$$\begin{aligned}
 8 + 0.2\text{H} &= 8 + j\omega L \\
 &= 8 + j \times 50 \times 0.2 \\
 &= (8+j10) \Omega
 \end{aligned}$$

Exercise

Exercise: 9.1, 9.2, 9.5, 9.6, 9.8, 9.9, 9.11, 9.13, 9.16, 9.20, 9.23, 9.24, 9.25, 9.35, 9.39, 9.42, 9.43, 9.44, 9.59, 9.60