


15 February, 2026



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
Spring 2026 Semester
CSE209 Electrical Circuits, Section-8, Class Test-1
Marks:10
Time: 25 minutes

ID#	20251-60-096	Name	Abdul Motalib Galib
-----	--------------	------	---------------------




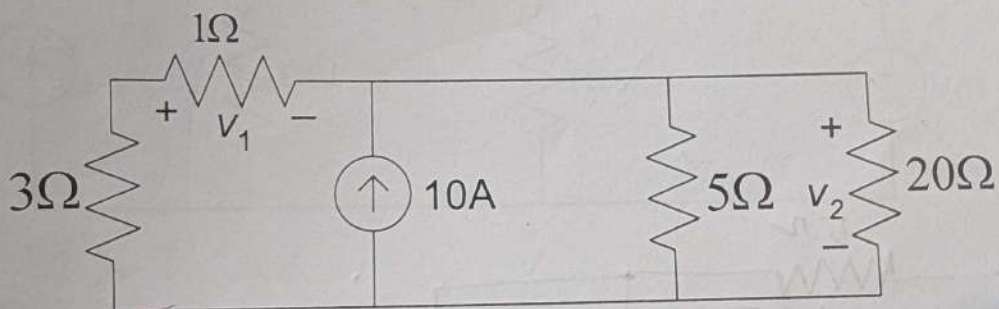
1. Calculate V_1 and V_2 in the following circuit using current division rule. [CO1, Mark: 5]



for V_2 apply current division rule,

15 February, 2026

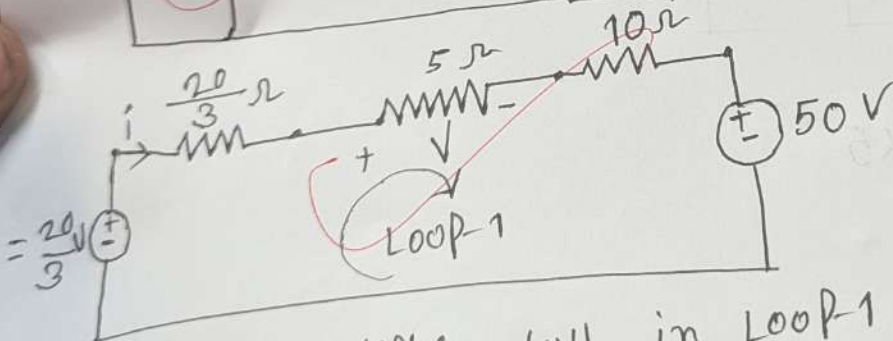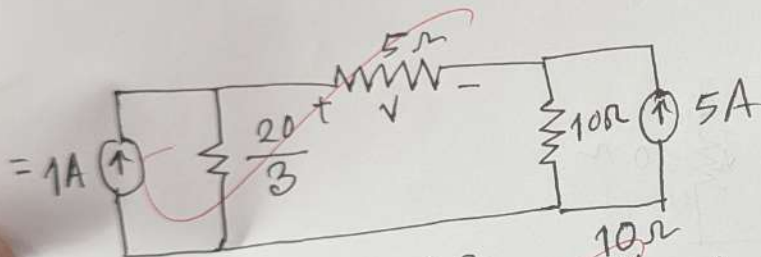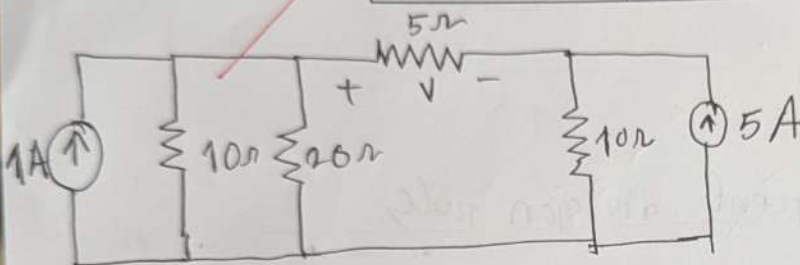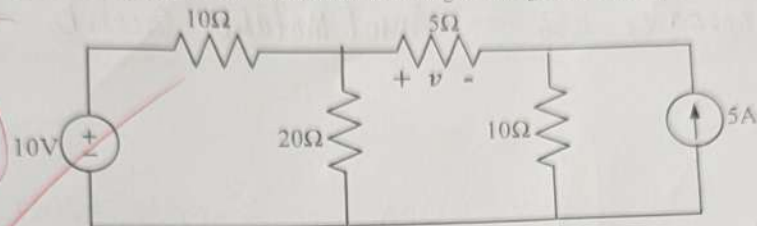2. Using Source Transformation, find v in the following circuit. [CO2, Mark: 5]



Apply KVL in Loop-1

$$\rightarrow -\frac{20}{3} + \frac{20}{3}i + 5i + 10i + 50 = 0$$

$$\rightarrow -\frac{20}{3} + \frac{65}{3}i + 50 = 0$$

$$\rightarrow \frac{130}{3} + \frac{65}{3}i = 0$$