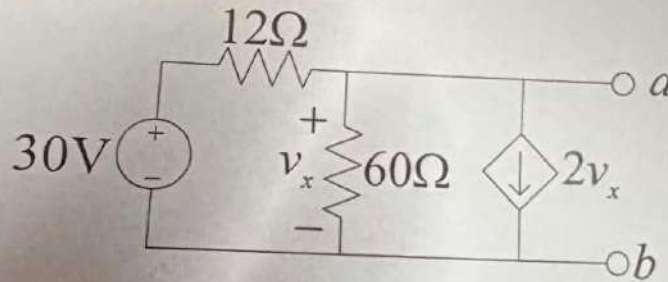


Course: CSE 209 Electrical Circuits, Section-8
Instructor: Musharrat Khan, Senior Lecturer, CSE Department
Full Marks: 30
Time: 1 Hour and 20 Minutes

Note: There are FIVE questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.


1. Determine the Norton's equivalent of the following circuit with respect to terminals a and b . Also calculate the maximum power.

[CO2,C3,
Mark:
6+1=7]




2. Determine Z_{eq} and I for the following circuit.

[CO1,C2,
Mark: 5]

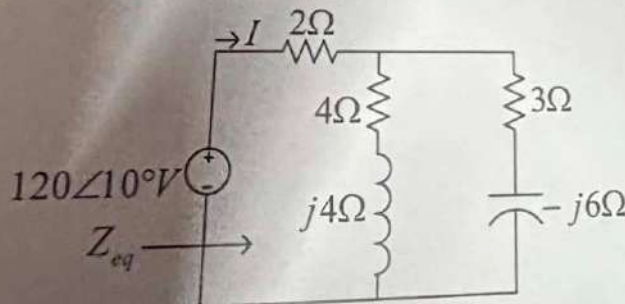

3. Using source transformation, find I_x in the following circuit.


[CO3,C3,
Mark:6]

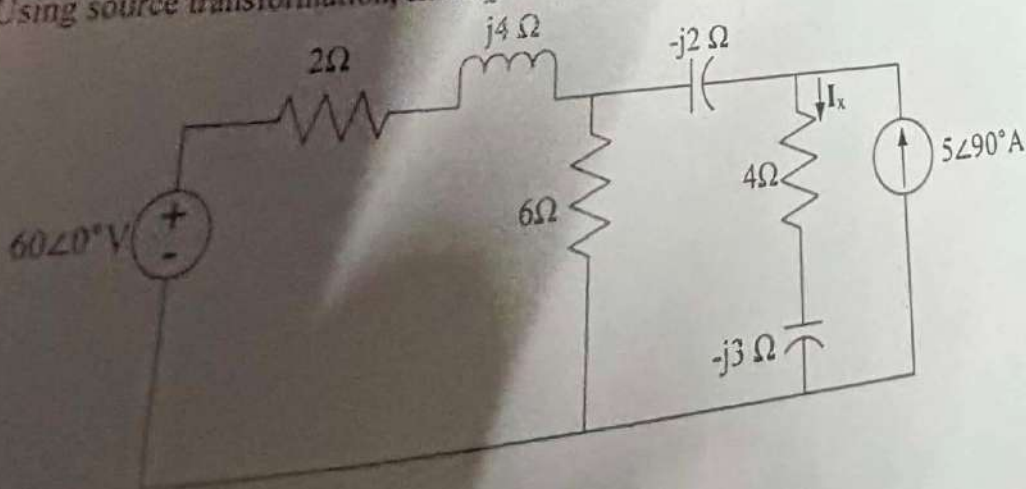

26 April, 2026

4. Using nodal analysis, compute V_1 for the following circuit.

[CO3,C3,
Mark:6]

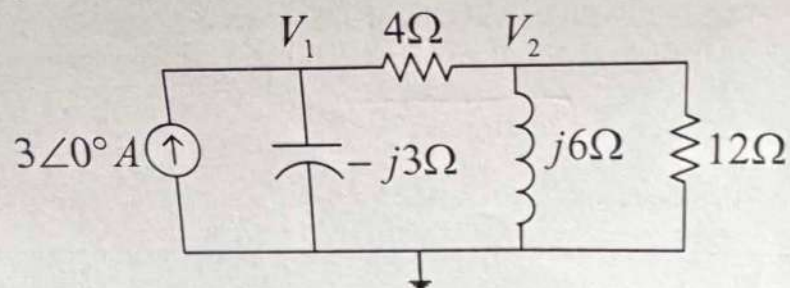

5. $v(t) = 200 \cos(\omega t - 10^\circ)$, $i(t) = 8 \cos(\omega t + 30^\circ)$. Determine the complex power, the apparent power, the real power, the reactive power, the power factor, and the load impedance.

[CO3,C3,
Mark:6]