

01 March, 2026




EAST WEST UNIVERSITY

Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Mid Semester Examination, Spring 2026 Semester


Course: CSE 209 Electrical Circuits, Section-8
Instructor: Musharrat Khan, Senior Lecturer, CSE Department
Full Marks: 30
Time: 1 Hour and 15 Minutes

Note: There are FIVE questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

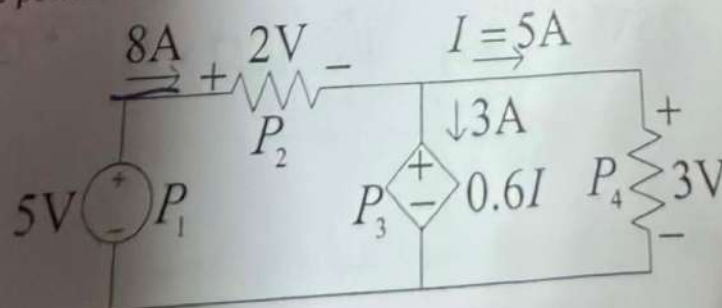1. Compute the power absorbed or supplied by each component of the following circuit. [CO1,C2, Mark: 5]



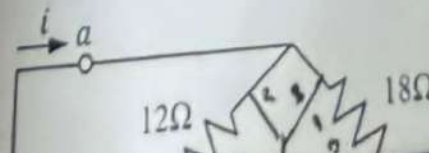2. Calculate R_{ab} and I in the following circuit using delta-wye transformation. [CO1,C3, Mark: 5]




$\Delta \rightarrow Y$

$$R_a R_b + R_b R_c + R_c R_a$$

01 March

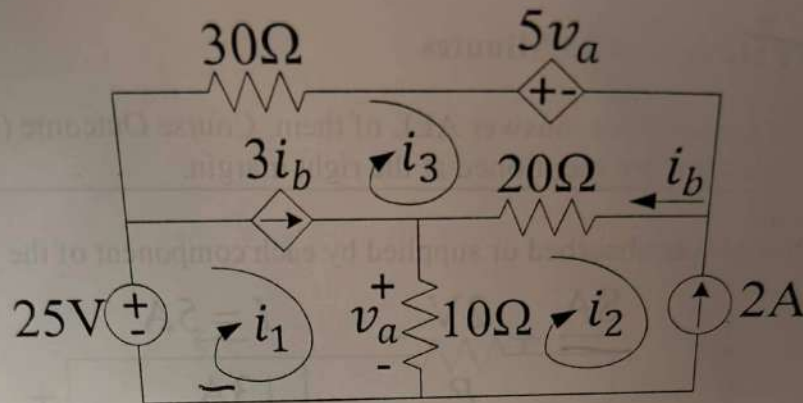4. Using mesh currents indicated in the circuit, determine i_1 , i_2 , and i_3 in the following circuit.



5. Using superposition theorem, find V_x and in the following circuit.

[CO2, C3, Mark: 8]

